

CSE115 / CSE503

Introduction to Computer Science I

Dr. Carl Alphonc
343 Davis Hall
alphonc@buffalo.edu

Office hours:

Tuesday 10:00 AM – 12:00 PM*

Wednesday 4:00 PM – 5:00 PM

Friday 11:00 AM – 12:00 PM

OR request appointment via e-mail

**Tuesday adjustments: 11:00 AM – 1:00 PM on 10/11, 11/1 and 12/6*

Today

Announcements: Scientista & ACM / Notetaker

Polls

Gates

Memory

Basic computer organization

Coming up

Instruction decoding

Fetch/Decode/Execute cycle

Low-level and high-level languages

Expressions and objects

Scientista meeting

Th @ 4:30

Davis 1st floor lounge

facebook.com/ubscientista

FREE FOOD!!

ACM meeting

Th @ 5:30

Davis 2nd floor lounge

ubacm.org

No free food, BUT BBQ Fri!

Notetaker request:

Thanks to everyone: no
more volunteers
needed!

POLL

Until we do an interactive exercise or a poll,
turn off and put away electronics:

cell phones

paggers

laptops

tablets

etc.

REVIEW

Physical reality:



WIRE

Carries a HIGH voltage or a
LOW voltage


Logical view:




WIRE

Carries a 1 or a 0

Controlling flow (normally open)

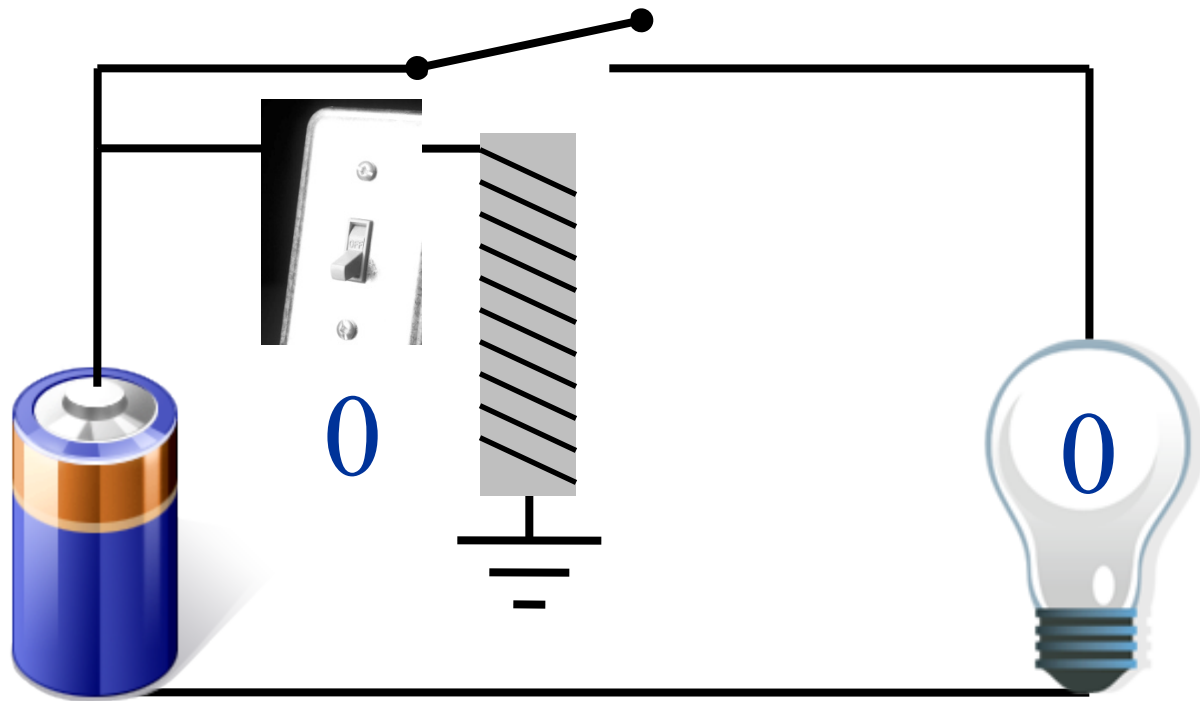


Controlling flow (normally open)

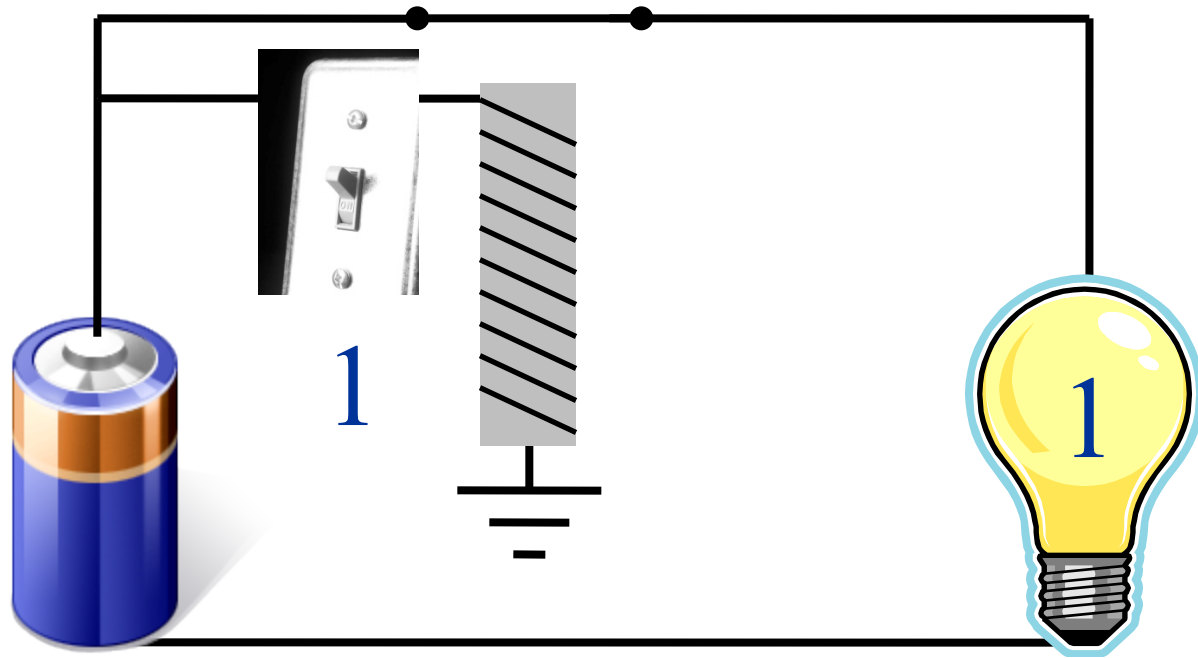


Interesting links

<http://history-computer.com/ModernComputer/Basis/relay.html>


Two in a row (in series)?

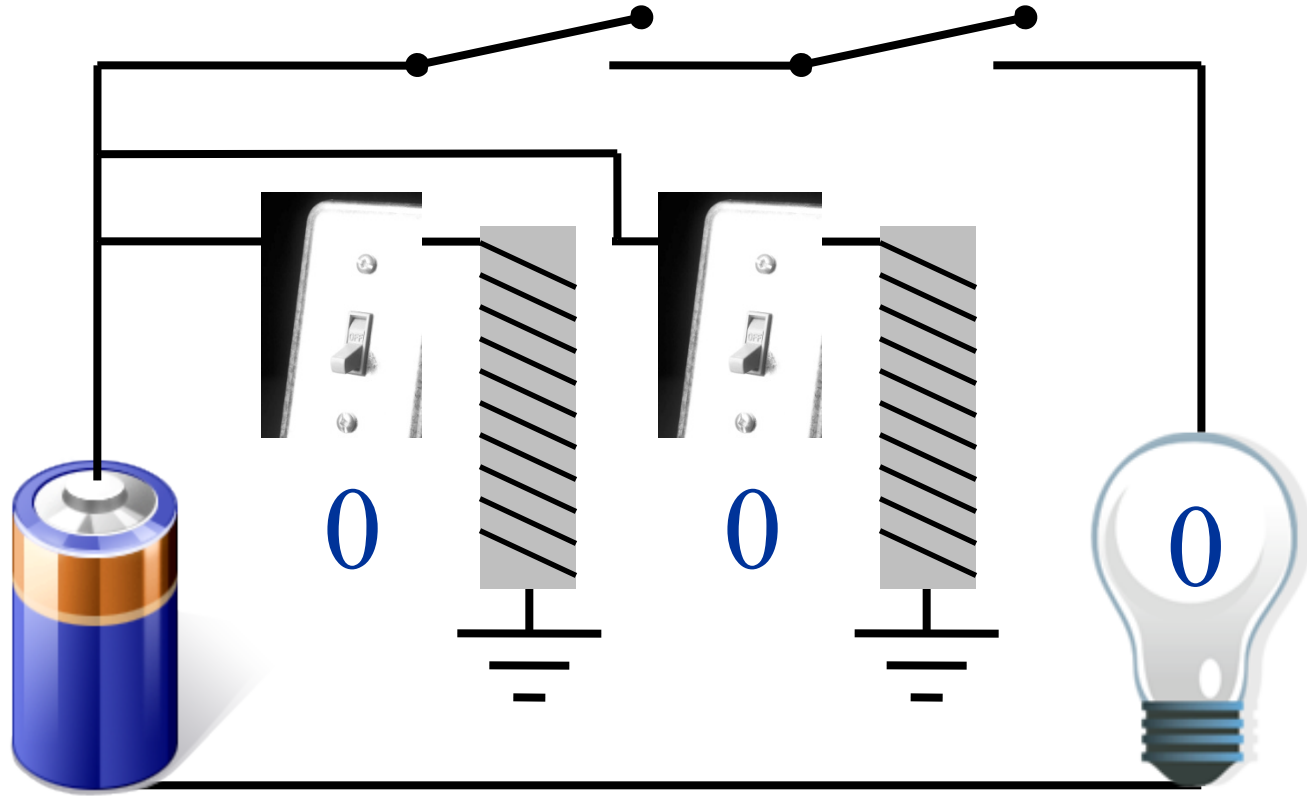


Two in a row (in series)?

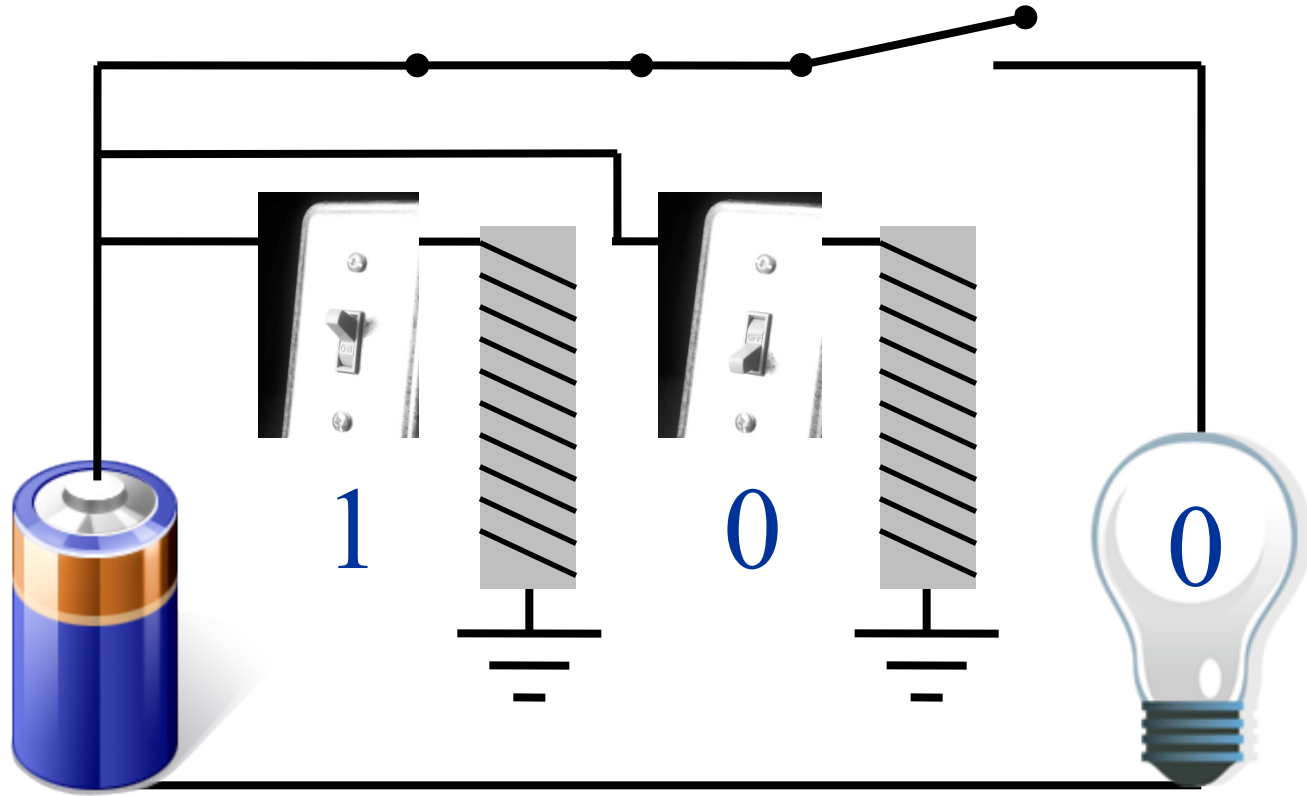


Two in a row (in series)?

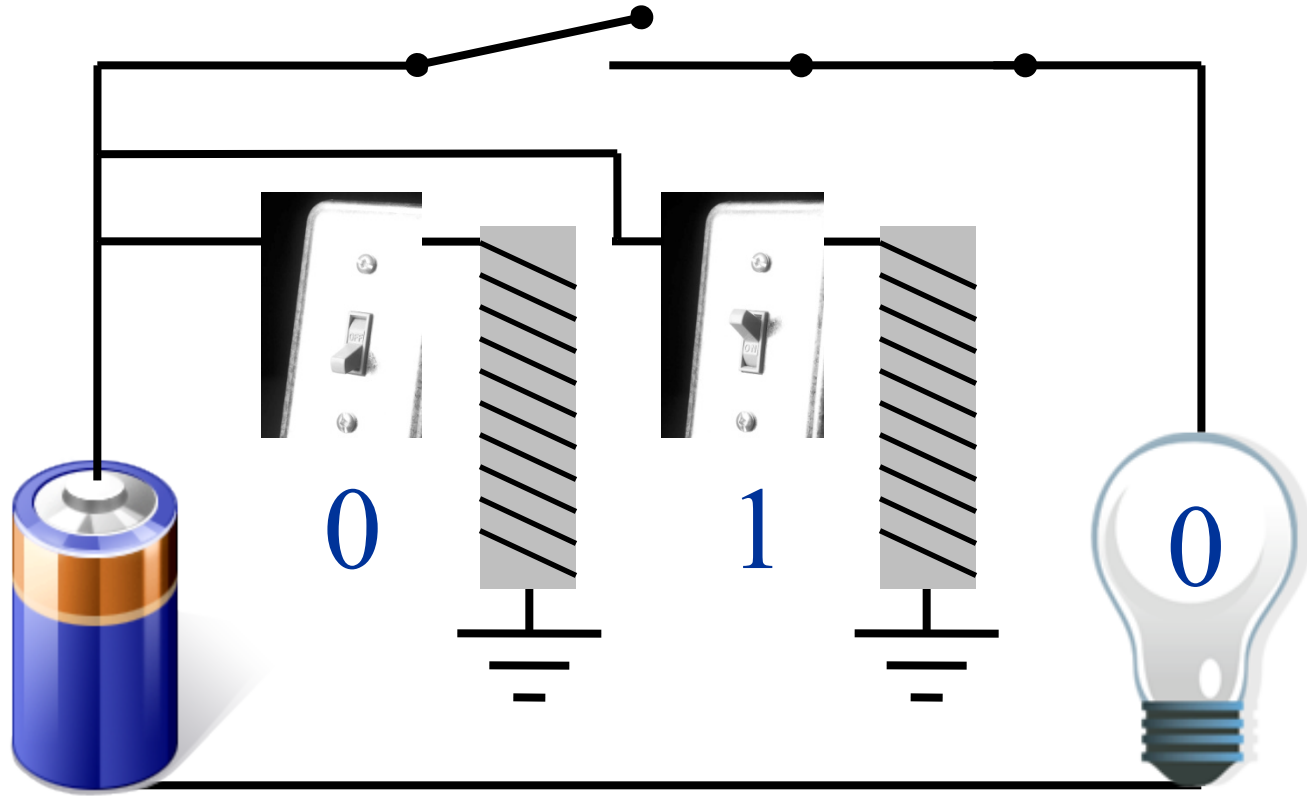

Two in a row (in series)?

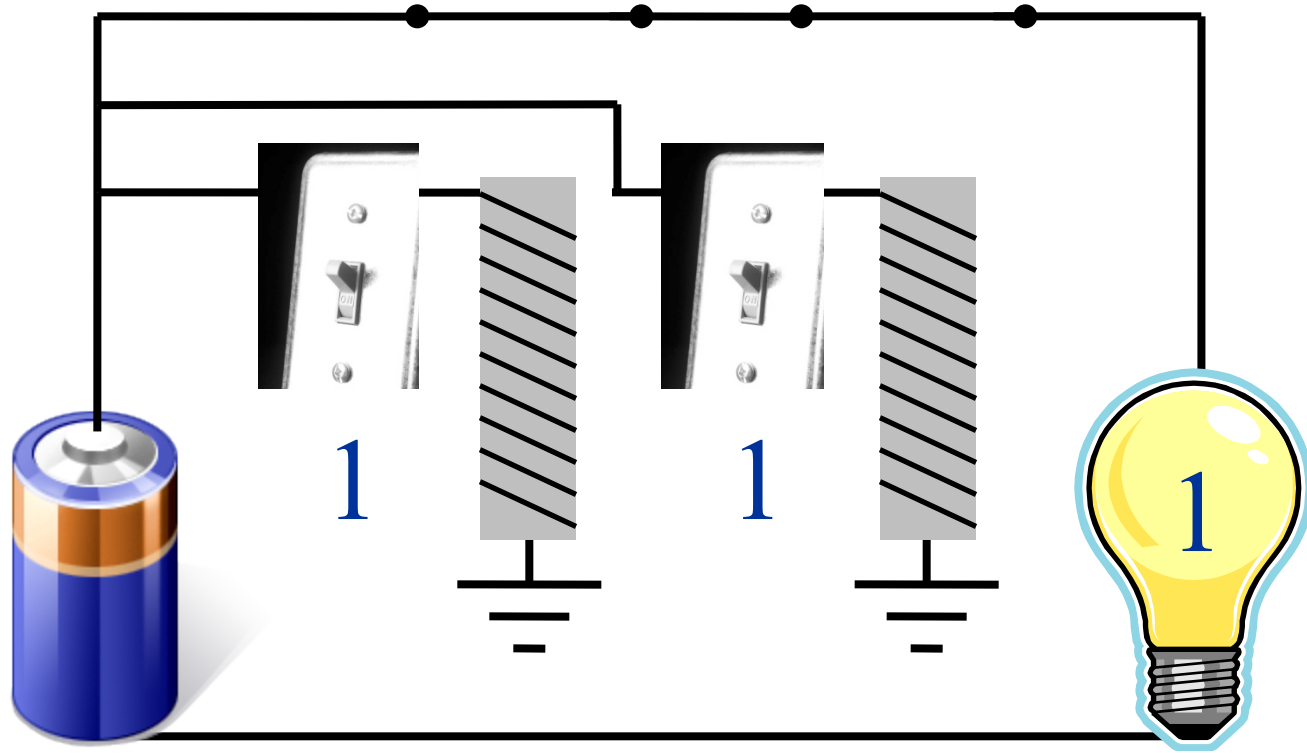

AND gate

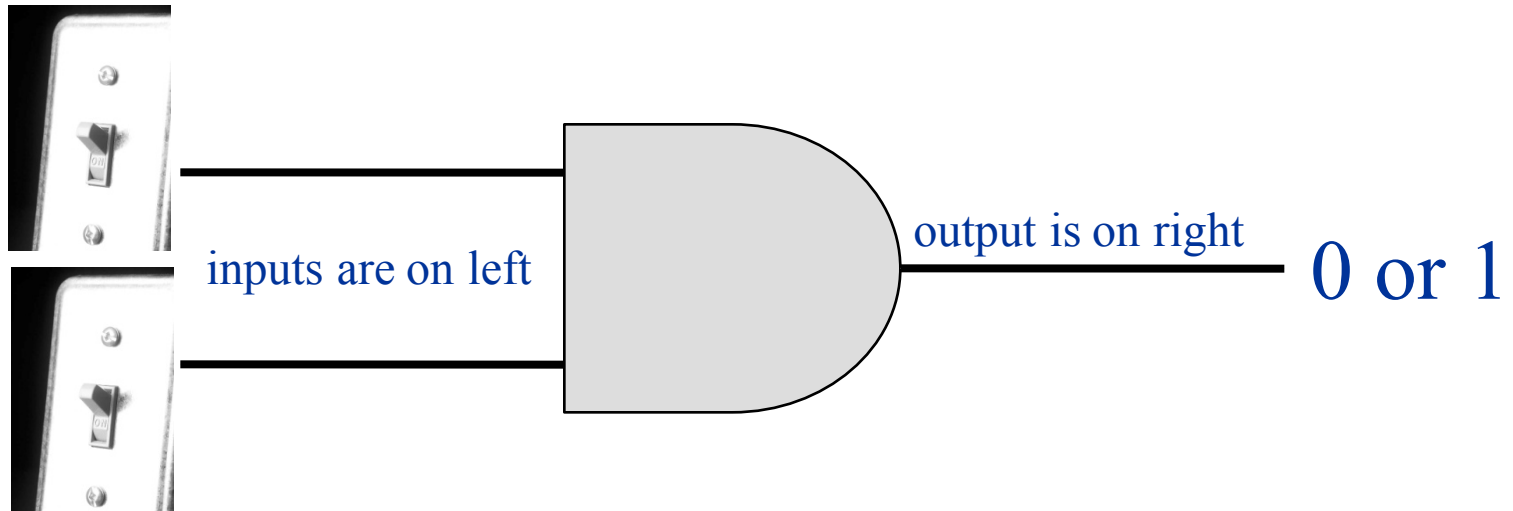

For which input values is output 1?


For which input values is output 0?

Truth table for AND


Input 1	Input 2	Output
0	0	0
0	1	0
1	0	0
1	1	1

MOVING ON


Two side by side (in parallel)?

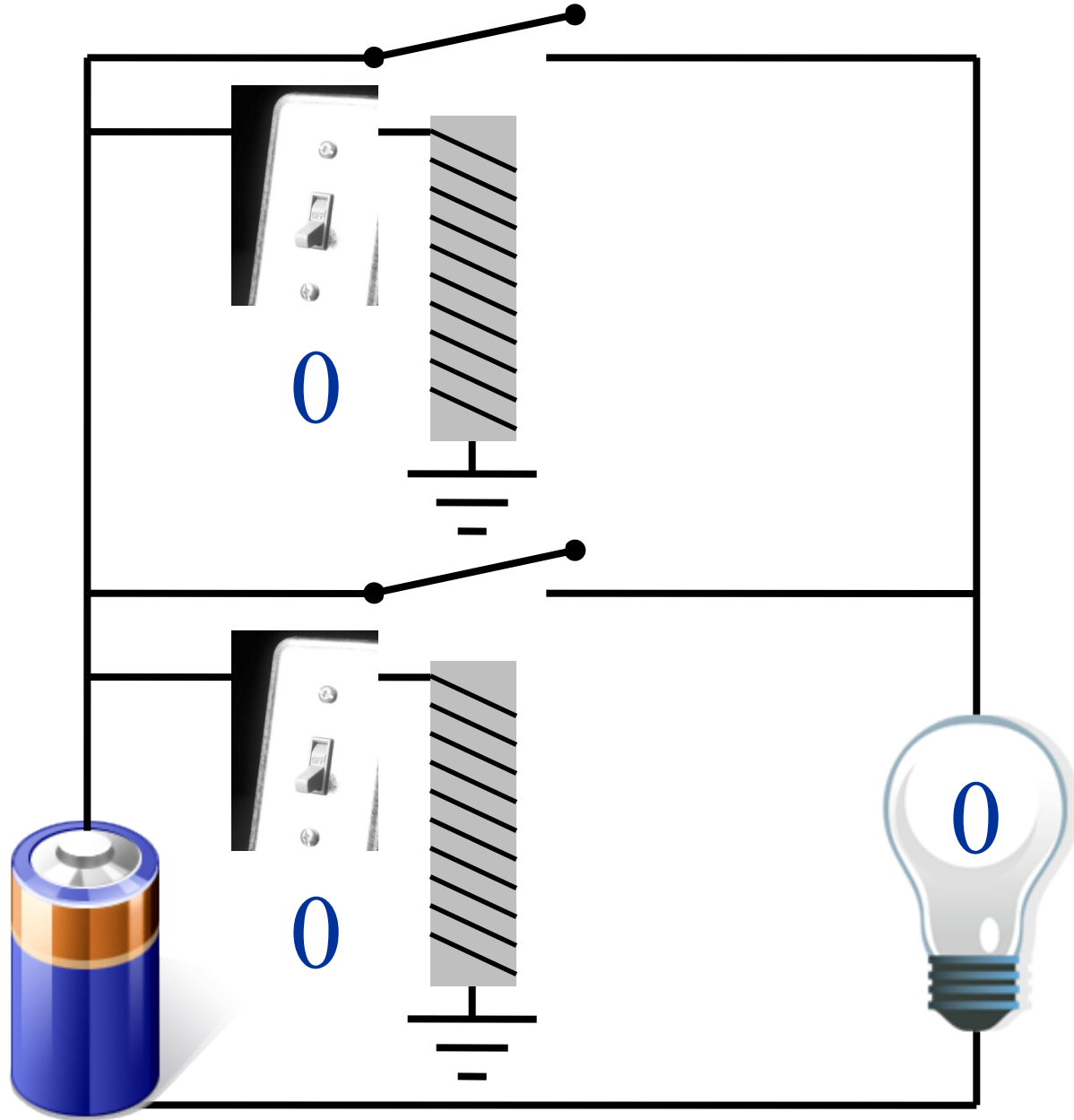


Two side by side (in parallel)?

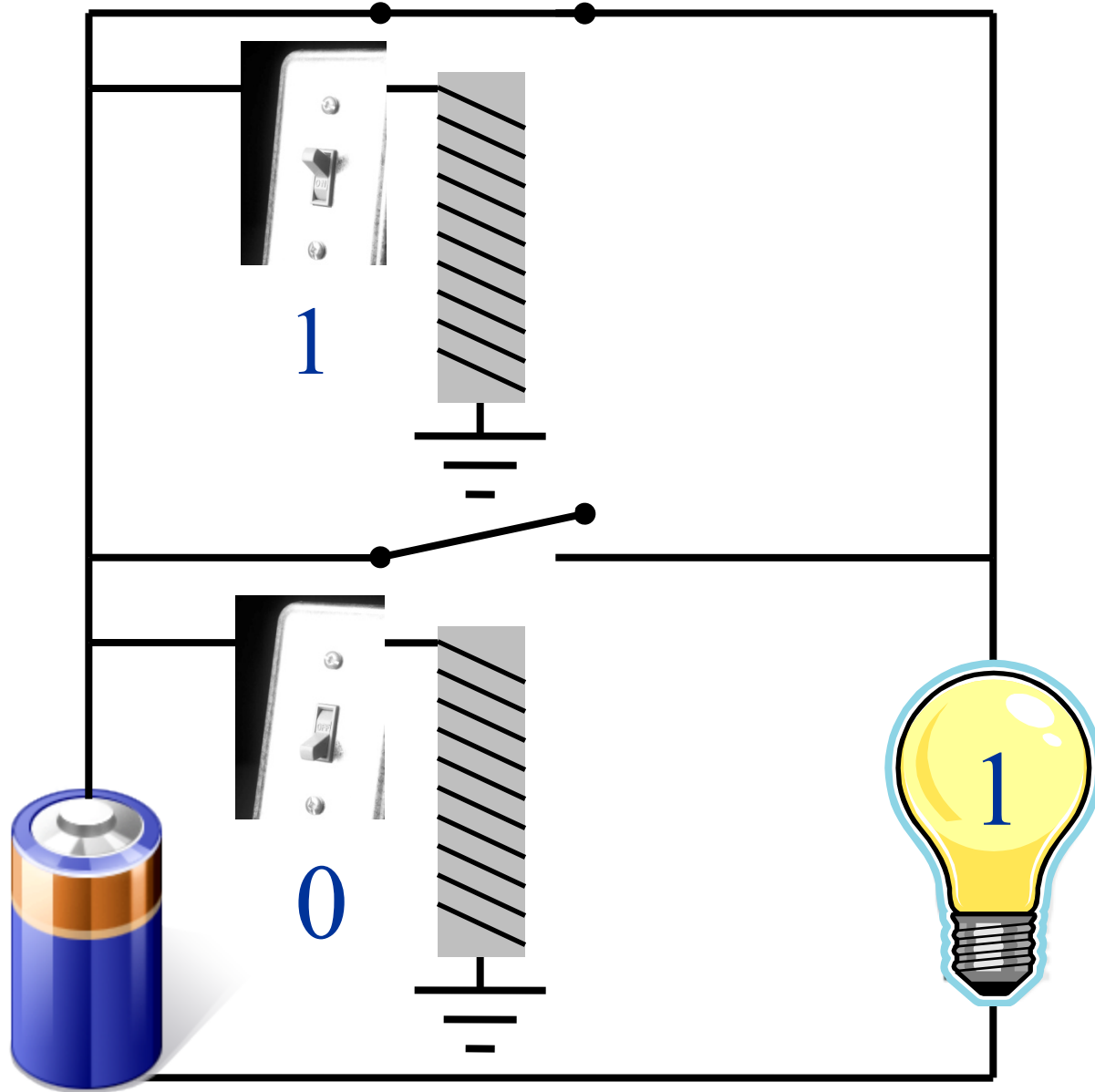


Two side by side (in parallel)?

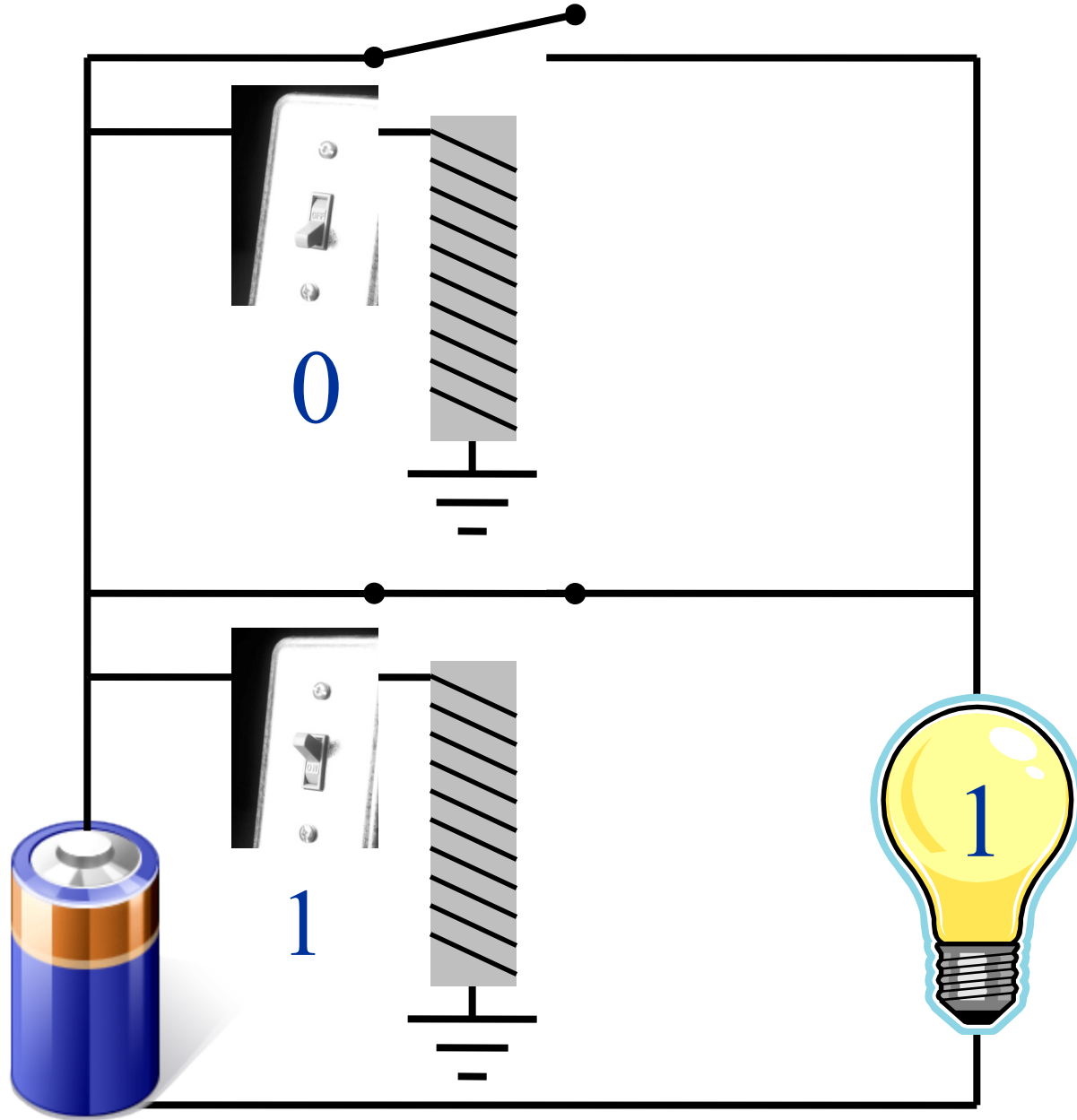

Two side by side (in parallel)?

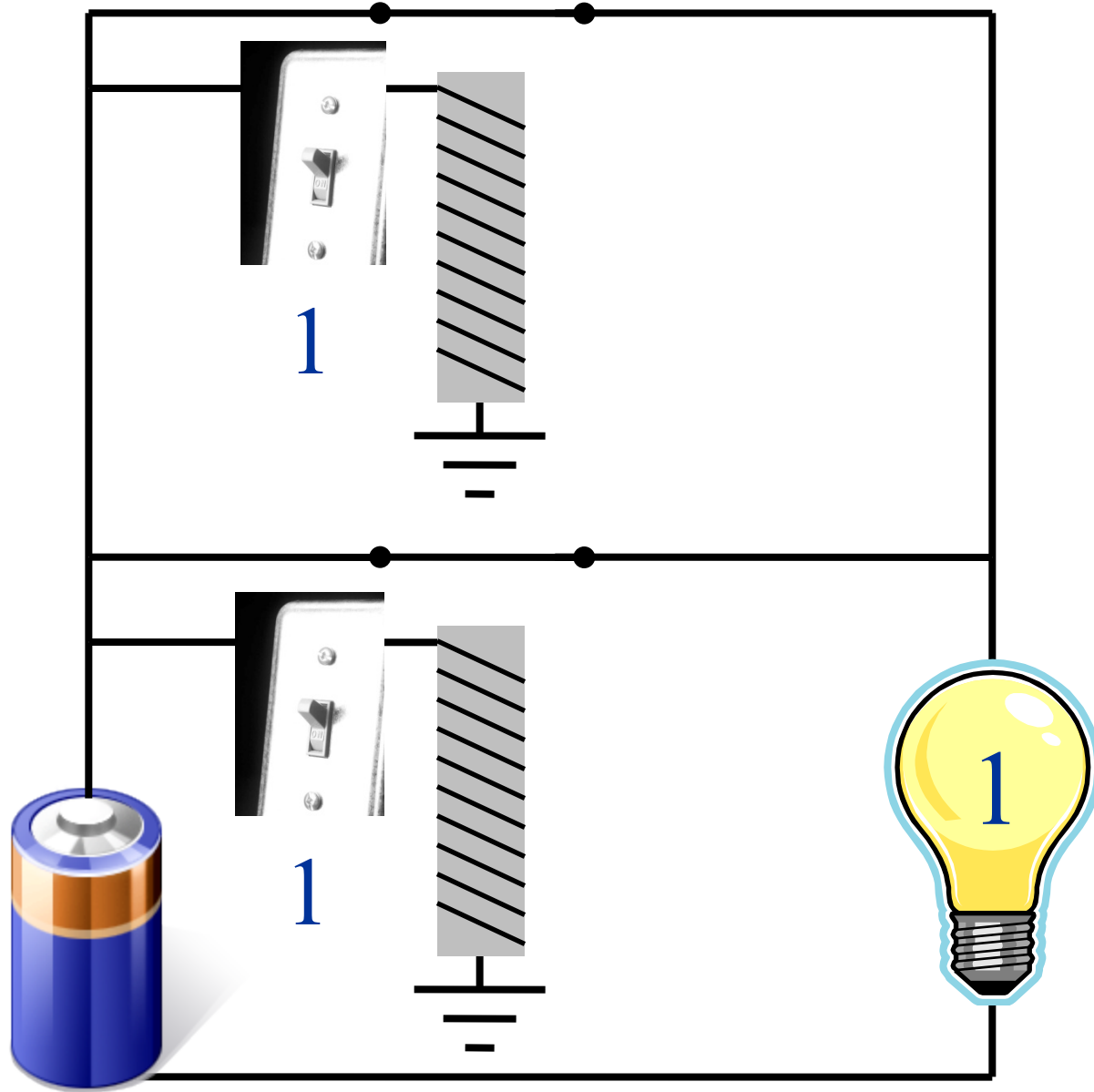

OR gate

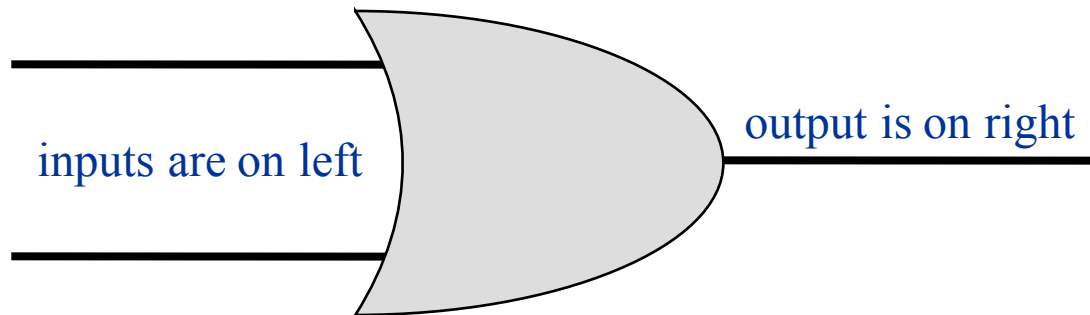


For which input values is output 1?

For which input values is output 0?


Truth table for OR

Input 1	Input 2	Output
0	0	0
0	1	1
1	0	1
1	1	1


Controlling flow (normally closed)

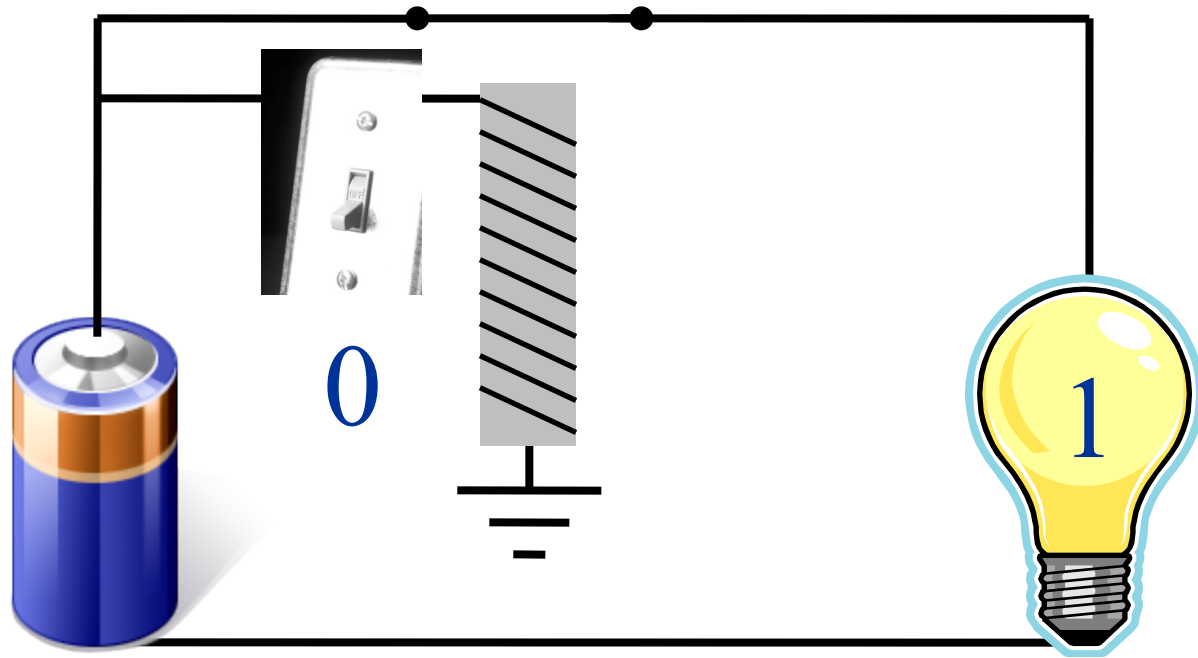

Controlling flow (normally closed)

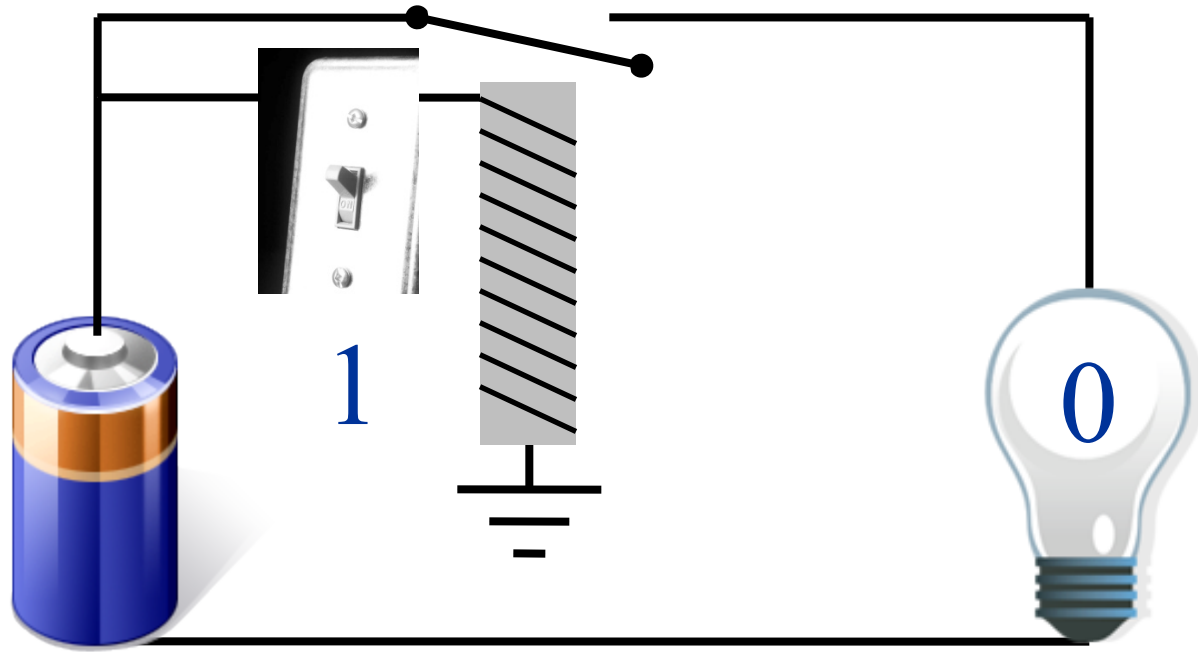

NOT gate

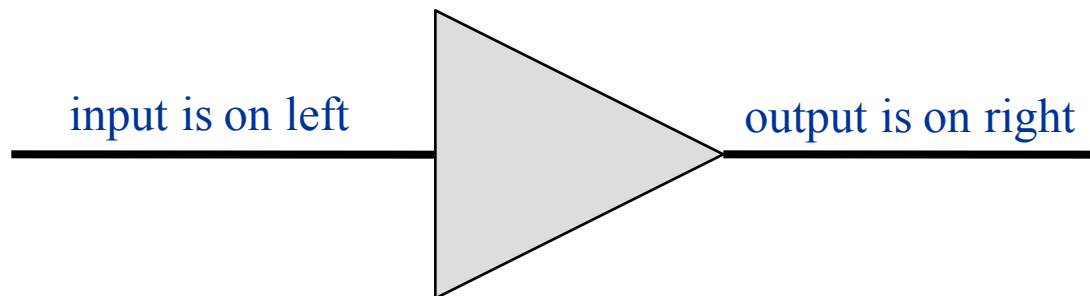

For which input value is output 1?


For which input value is output 0?

Truth table for NOT

Input	Output
0	1
1	0


MEMORY

Flip-flop (a bit of memory!)

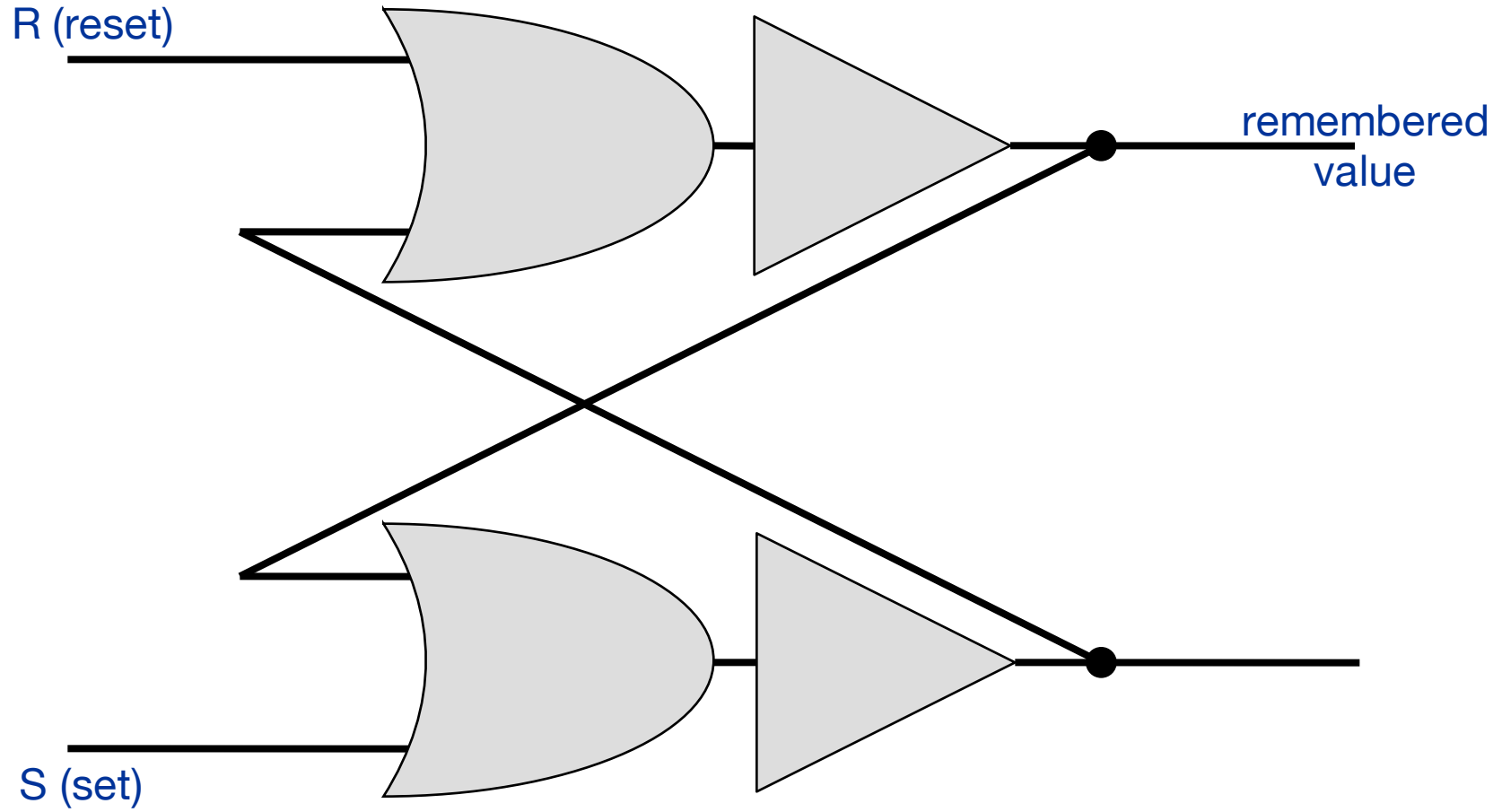

The normal value of both R and S is zero

R (reset) = 0

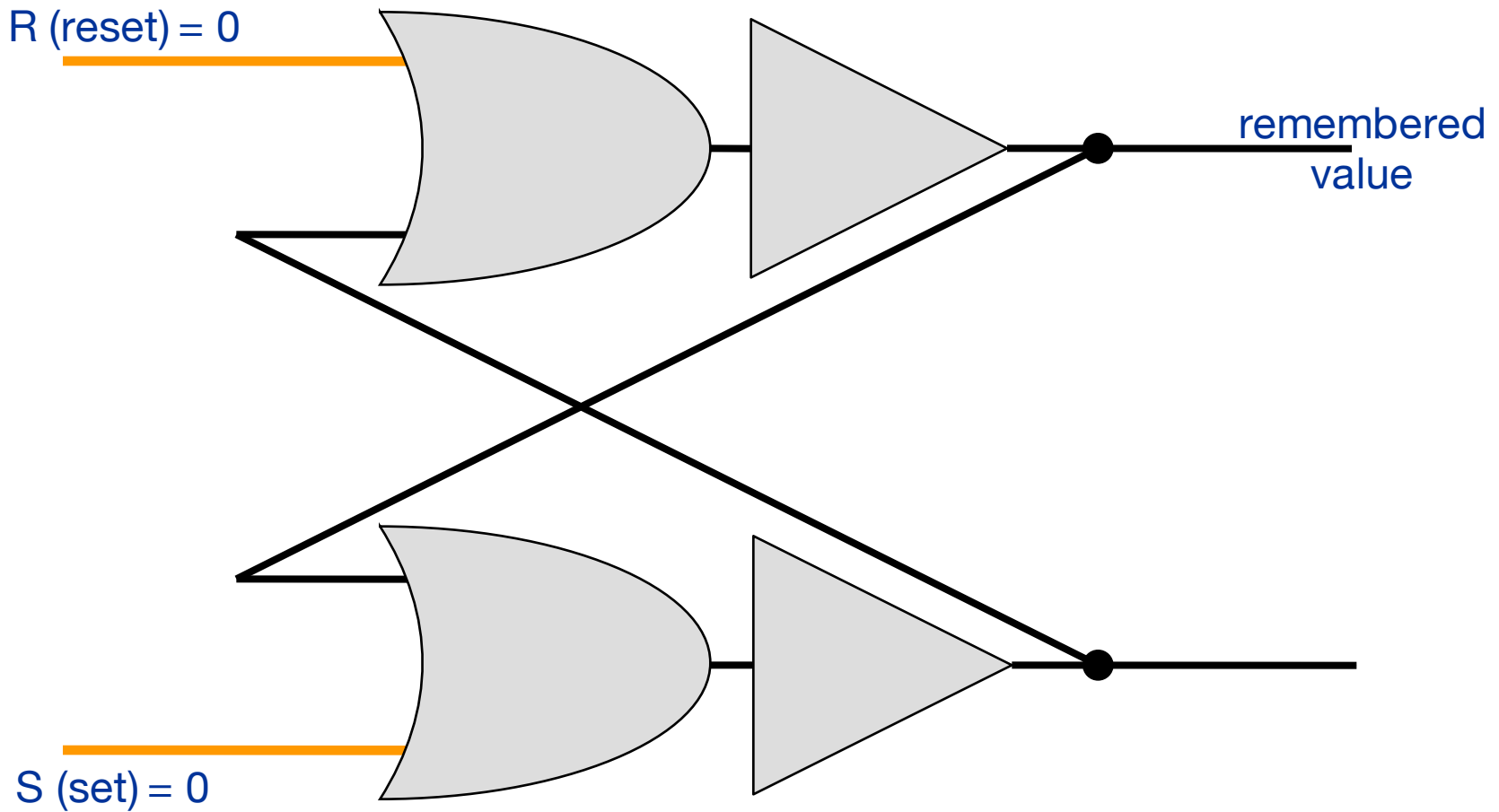


S (set) = 0

remembered
value

Setting the flip-flop.

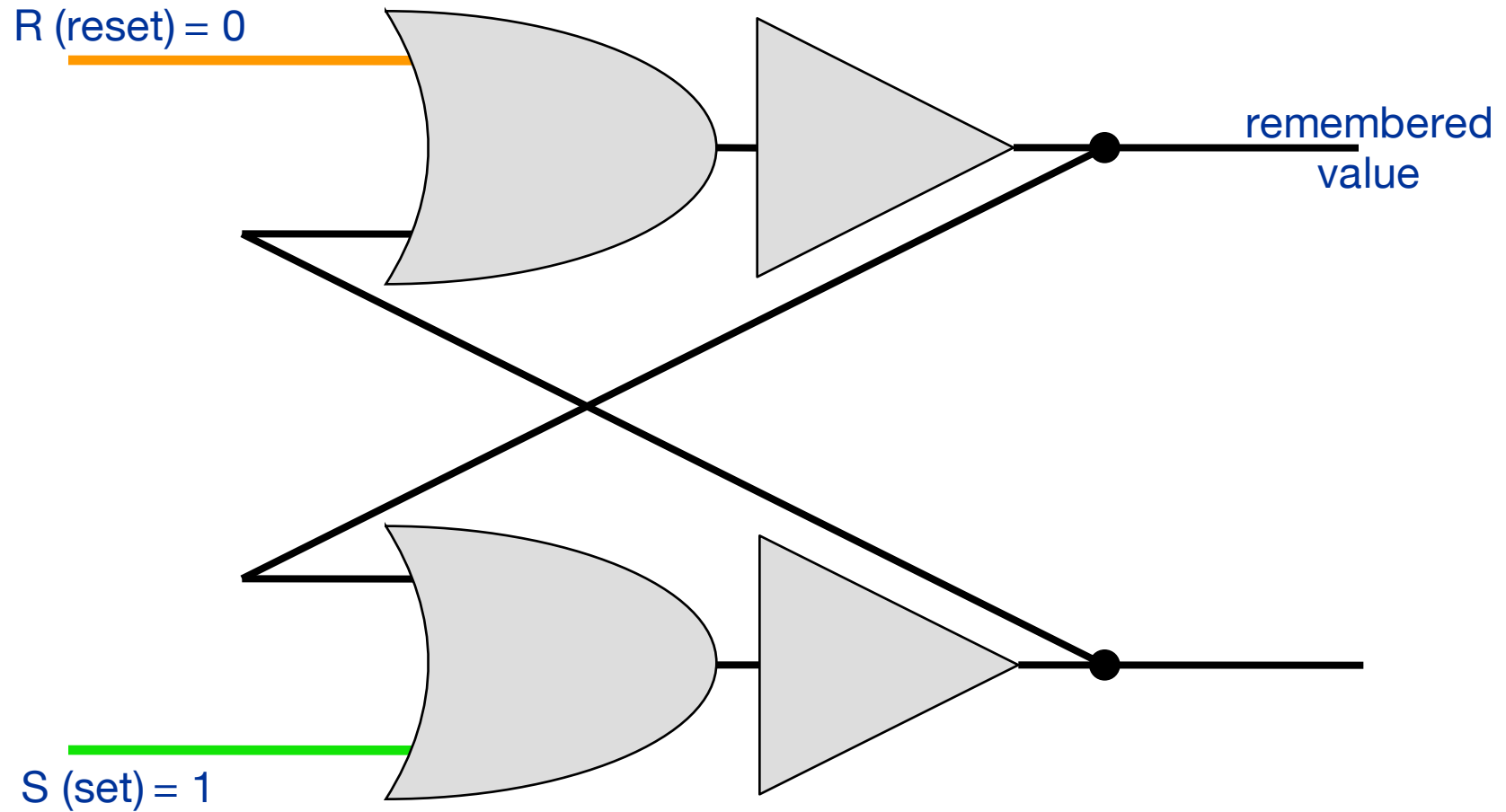
To store 1 in the flip-flop, we “raise” S to 1



Setting the flip-flop...


which makes the output of the OR gate 1

R (reset) = 0

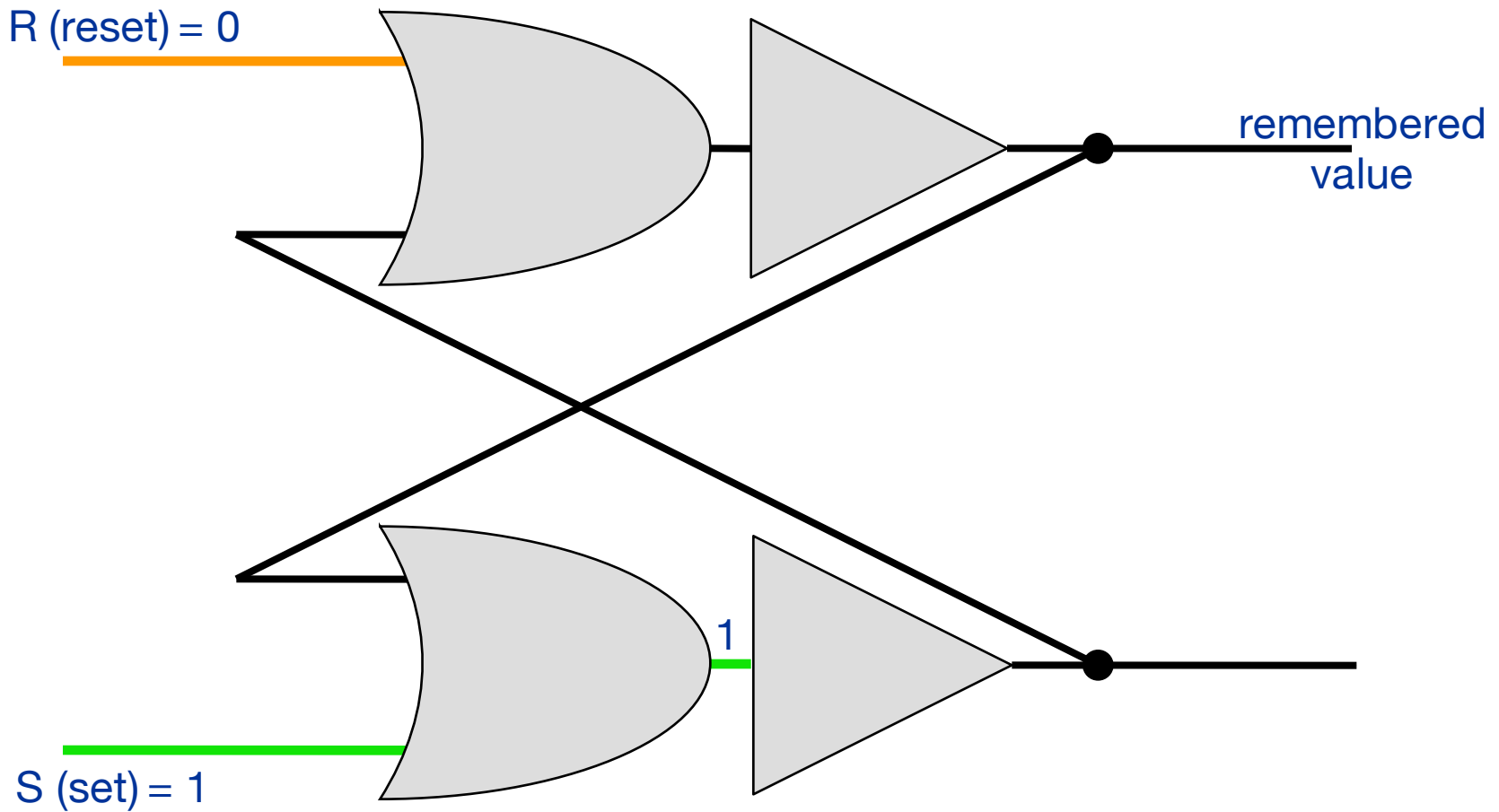


Setting the flip-flop.

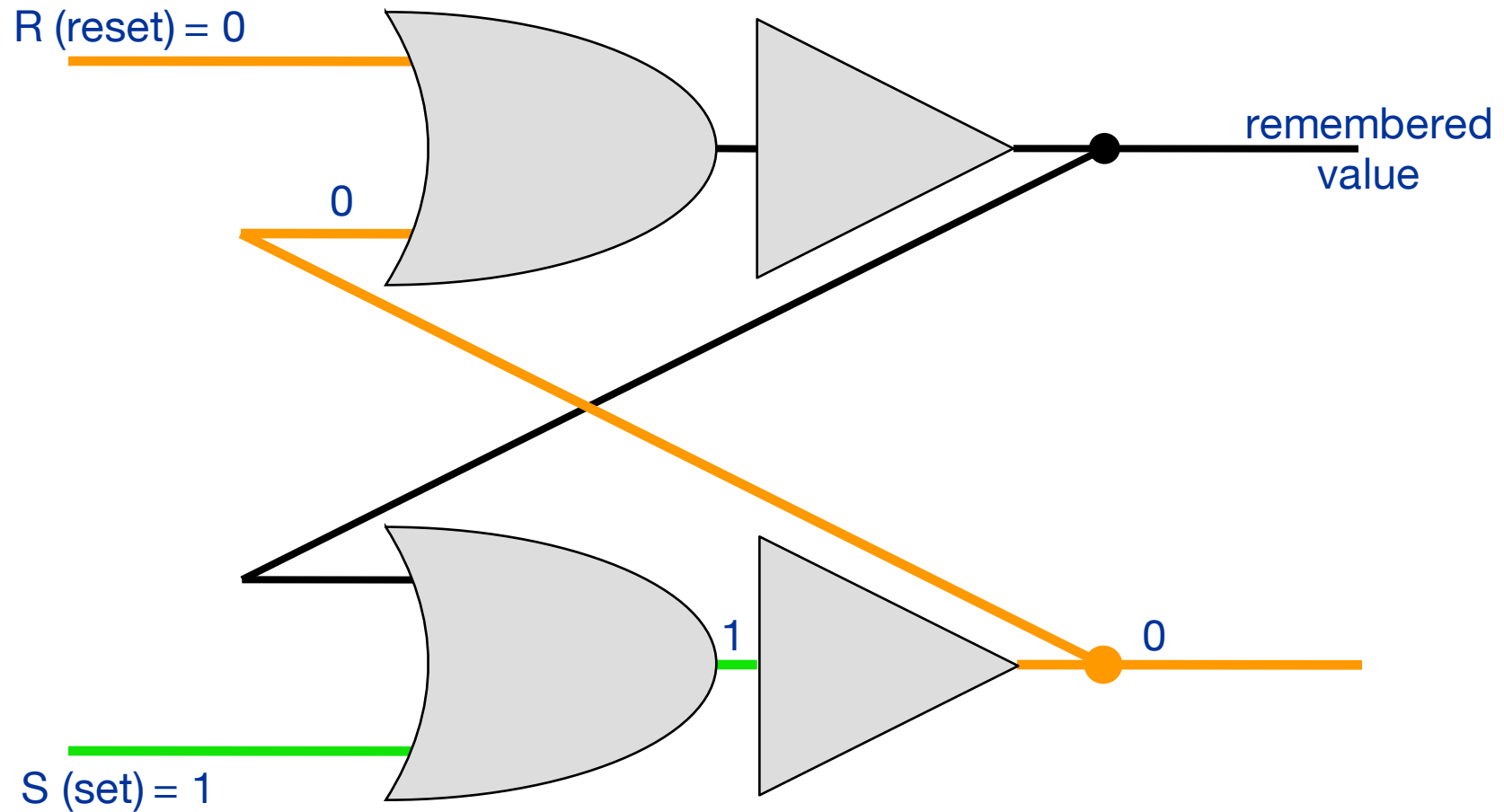
The NOT gate inverts this 1 value to 0, which becomes the second input to the upper OR gate.



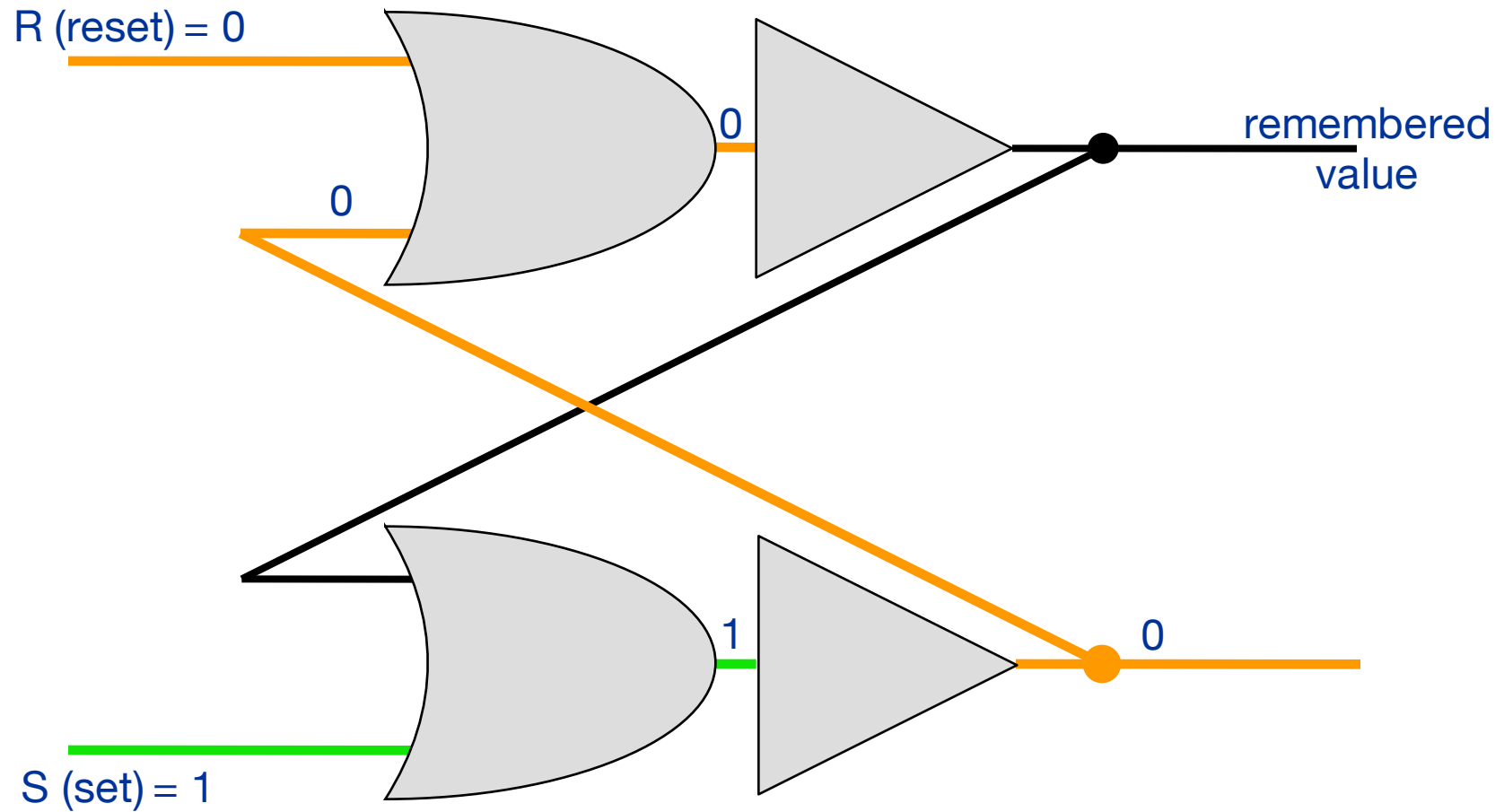Since both inputs of the upper OR gate are zero, its output is zero.




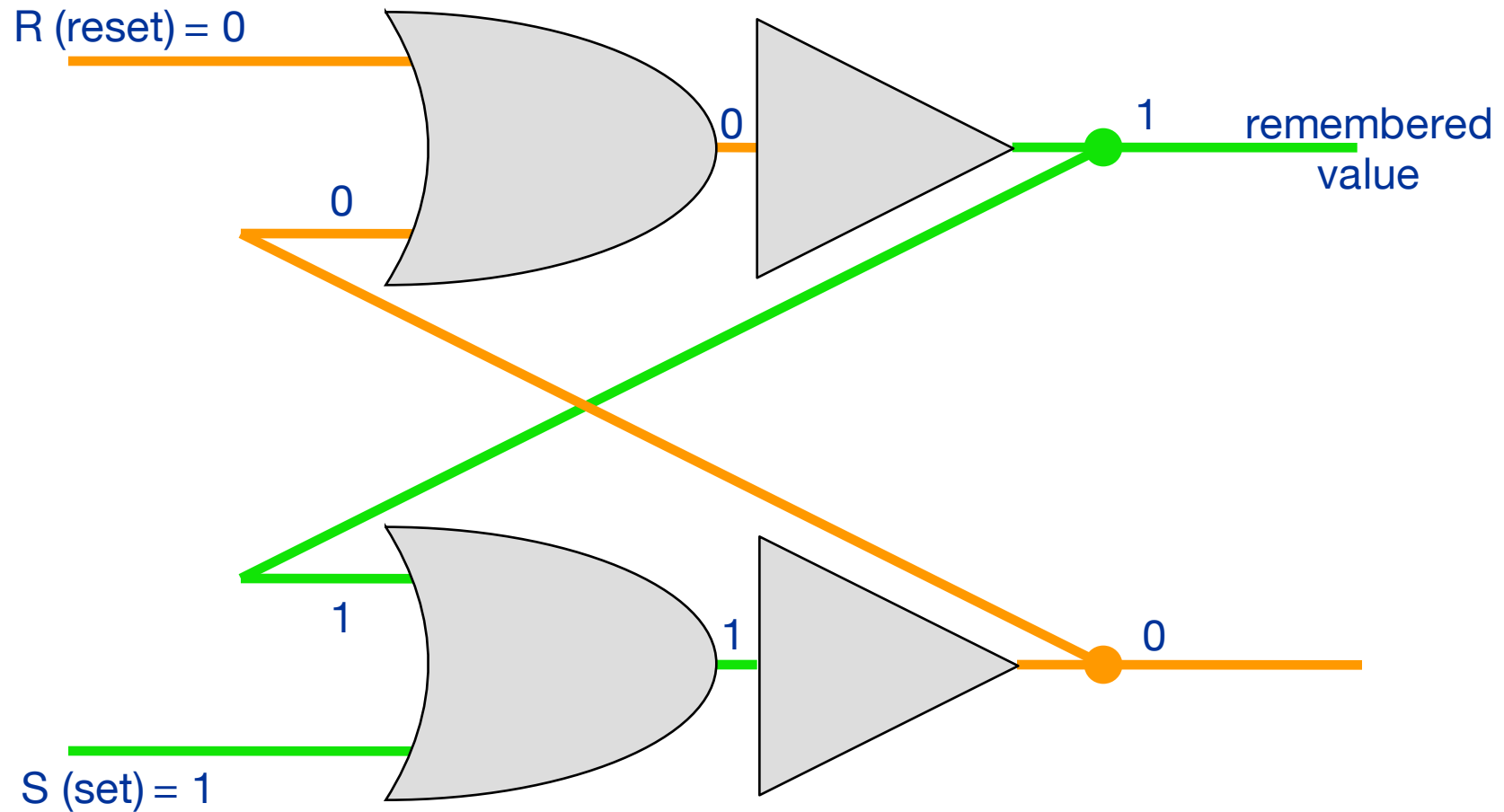The NOT gate inverts this 0 to a 1; this value becomes the second input to the bottom OR.



Because the output of the bottom OR gate will now stay at 1, we can lower S to zero, and the circuit will stay in a stable state, with 1 as the remembered value!


R (reset) = 0

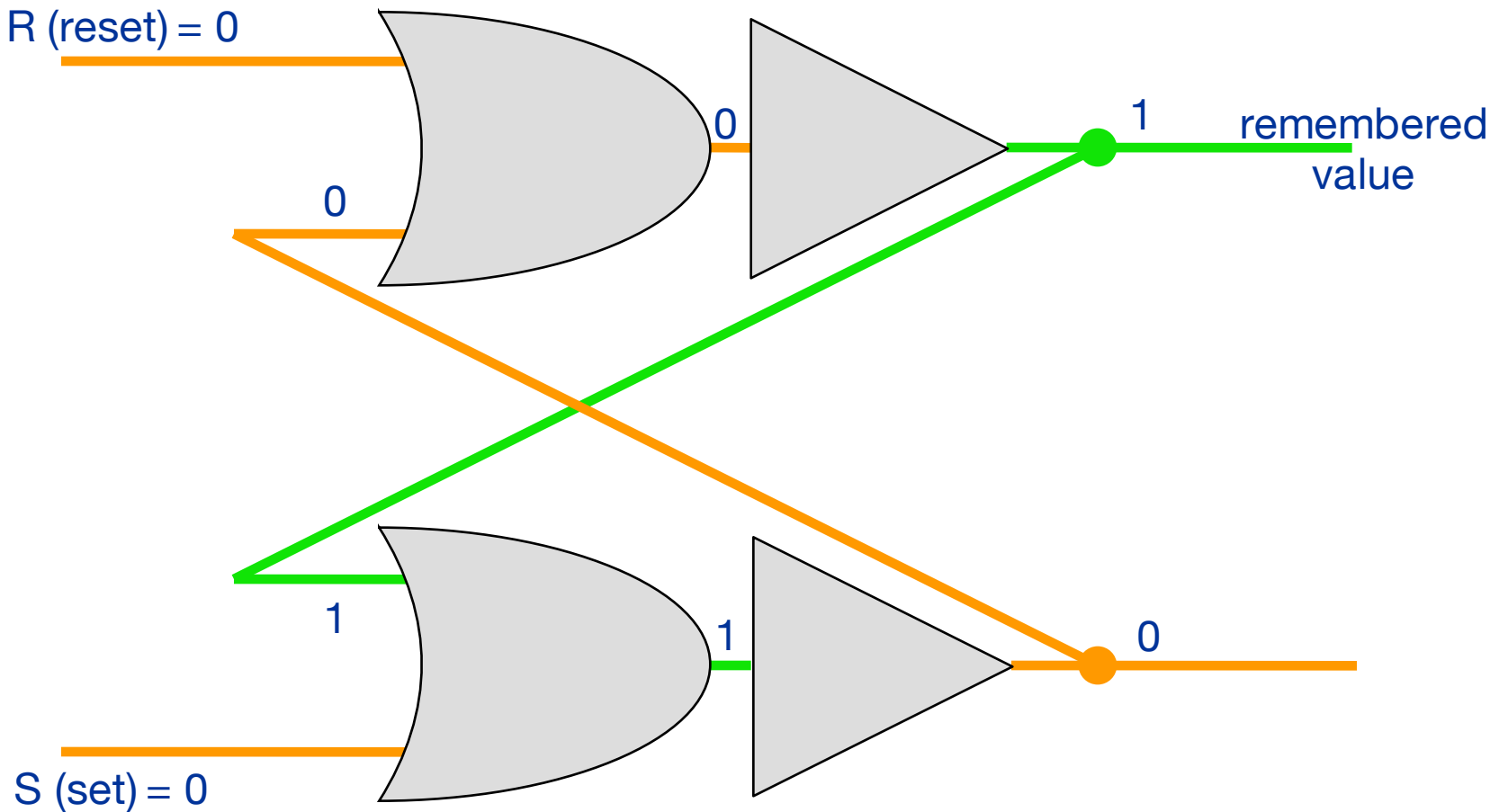

Setting the flip-flop

Resetting the flip-flop

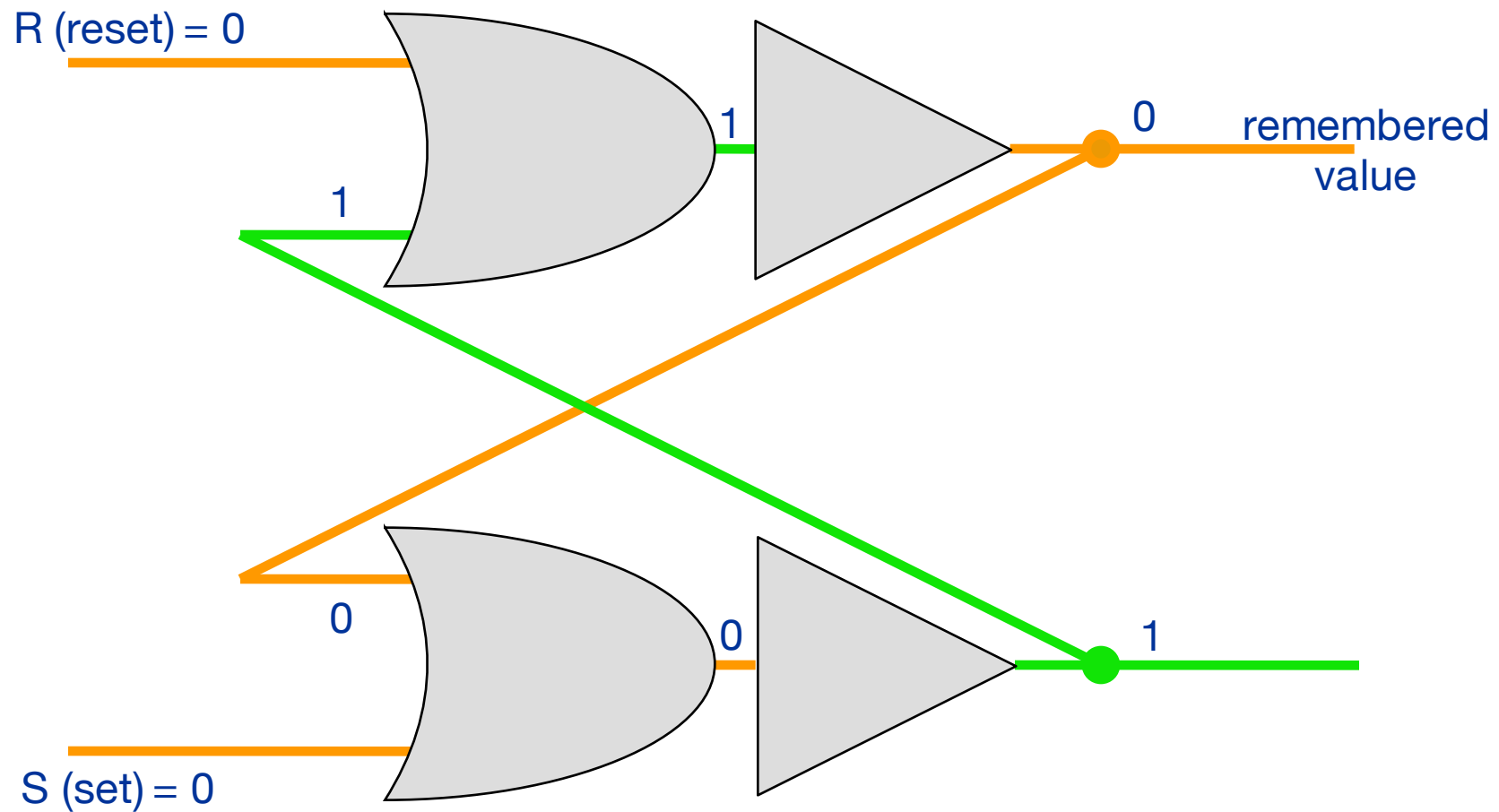Resetting the remembered value to zero is similar, except we raise, then lower, the value on R.



Recap

A sequence of bits (a.k.a. *bit string*) by itself does not carry meaning.

A bit string can be interpreted under a given representation scheme, which allows us to recover the encoded meaning.

Circuits made from simple gates let us store and manipulate bit strings.

1 flip-flop stores 1 bit
1 byte = 8 bits

Primary storage (2^x)

1 KB = 2^{10} bytes
(1,024 bytes)

1 MB = 2^{20} bytes
(1,048,576 bytes)

1 GB = 2^{30} bytes
(1,073,741,824 bytes)

Secondary storage (10^x)

1 kB = 10^3 bytes
(1,000 bytes)

1 MB = 10^6 bytes
(1,000,000 bytes)

1 GB = 10^9 bytes
(1,000,000,000 bytes)

For more info, see https://en.wikipedia.org/wiki/Binary_prefix

INSTRUCTION DECODING

Memory

Central Processing Unit (CPU)

Memory

Central Processing Unit (CPU)

Arithmetic Logic Unit (ALU)

Registers

Memory

Central Processing Unit (CPU)

Arithmetic Logic Unit (ALU)

Registers

General purpose (e.g. R1 – R16)

Special purpose (e.g. Program Counter and Instruction Register)

Computer Organization

Memory
(RAM)

Processor (CPU)

