

March 3, 2017



CSE 241

① Spring 2017

Mid term exam 3/13/2017

We will review next week
for this.

MSI Decoder:

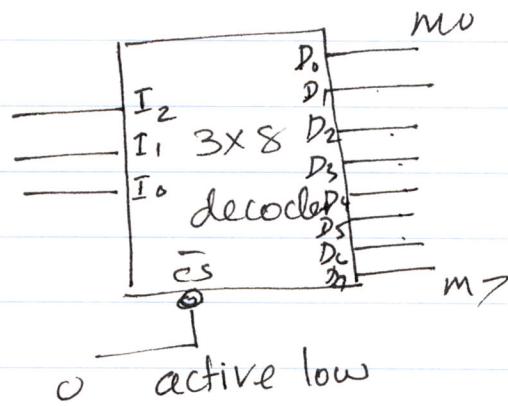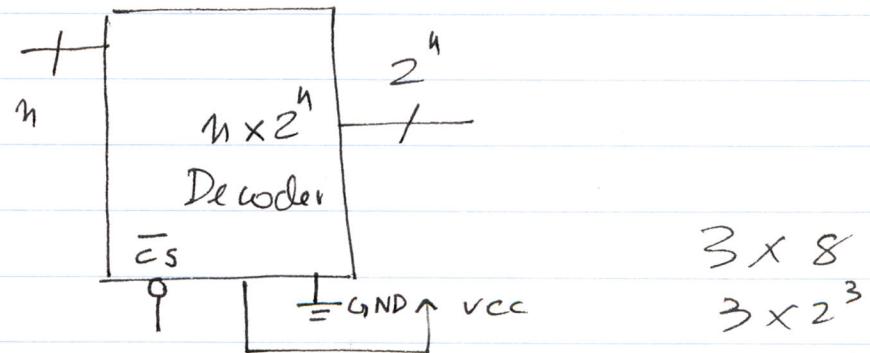

Normal inactive
state when
 $\bar{CS} = 1$

Function: $I_2 \ I_1 \ I_0 \quad D_0 \ D_1 \ D_2 \quad \bar{CS} = 1$

0	0	0	✓		
0	0	1	✗	✓	
0	1	0			✓

(2)


March 3 2017

Applications:

Implement a combinational circuit

$$f(A, B, C) = \sum (m_1, m_3, m_7)$$

$$= A'B'C + A'BC + ABC$$

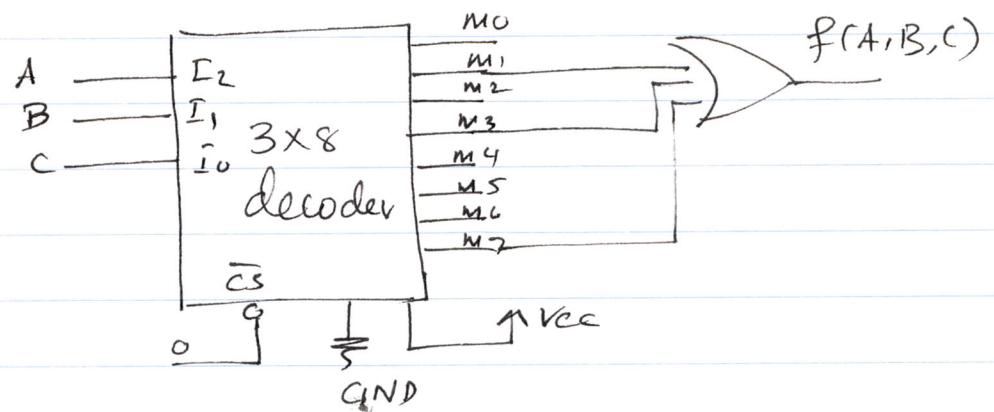


Implement a combinational circuit

$$f(w, x, y, z) = \sum (m_0, m_4, m_8, m_{11})$$

$$= w'x'y'z' + w'x'y'z + wx'y'z' + wx'yz$$

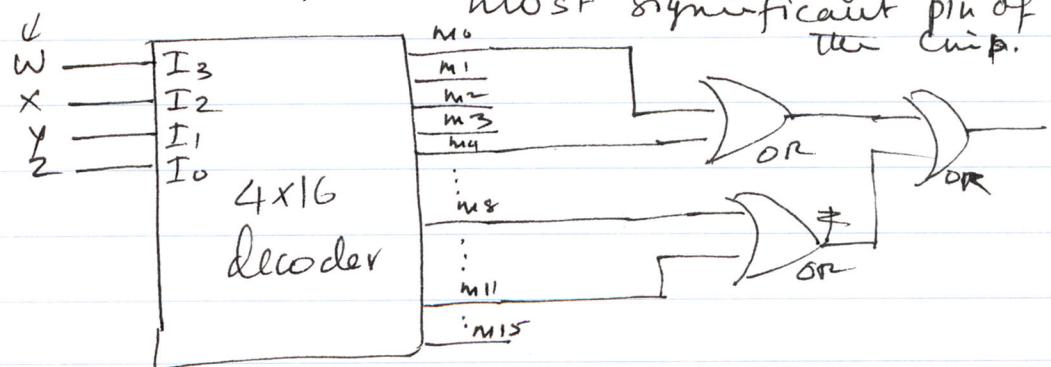most significant bit of input goes to the most significant pin of the chip.



74LS138 is part of your kit


It is a NAND output Decoder 3x8

(3)

Make a larger decoder with two or more smaller decoders.

Make a 4×16 decoder using 2 3×8 decoders.

4×16 decoder

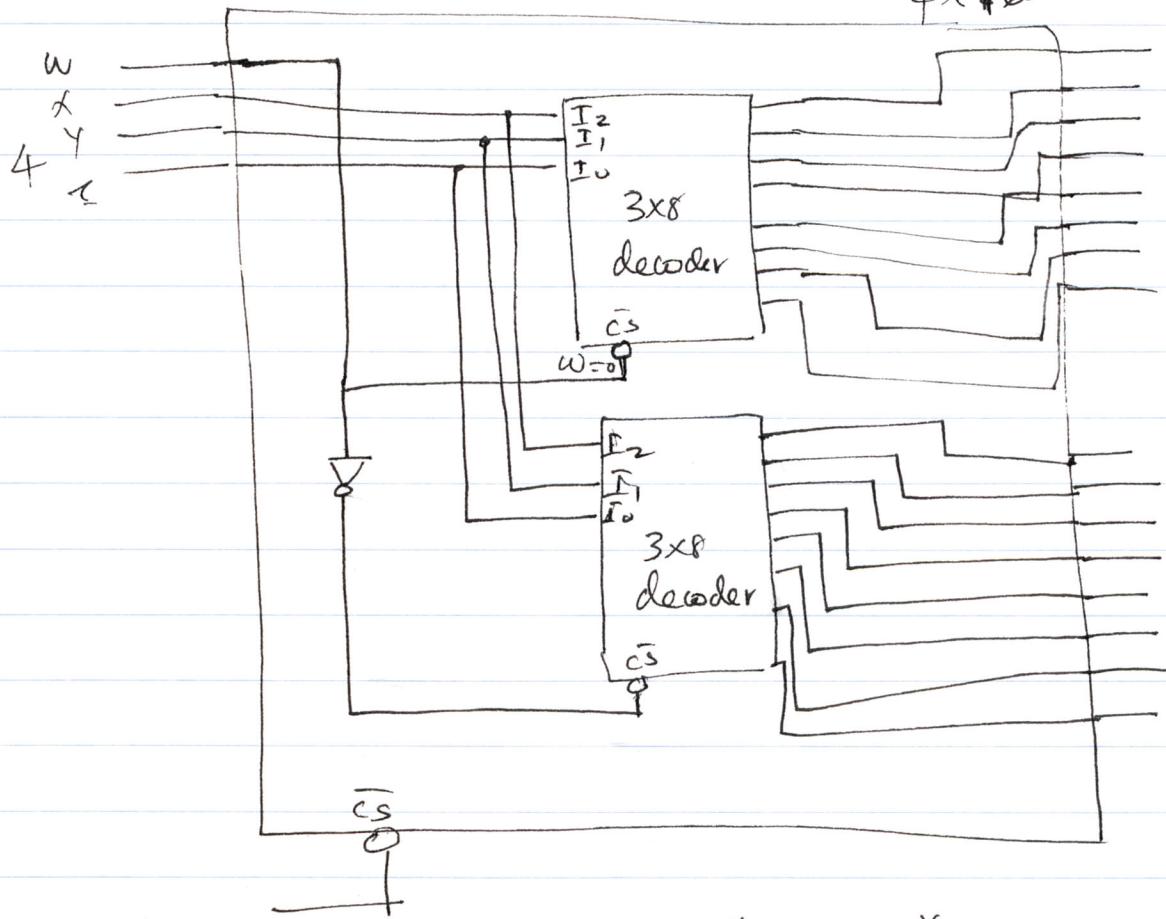

$w \quad x \quad y \quad z$

$w=0$	0	0	0	0
	0	0	0	1
	0	0	1	0
	0	0	1	1
	0	1	0	0
	0	1	0	1
	0	1	1	0
	0	1	1	1

top chip

3×8

bottom half



$w=1$

bottom chip

3×8

Mux
④

Multiplexer Mux

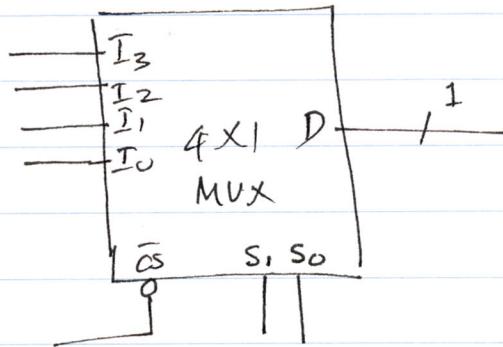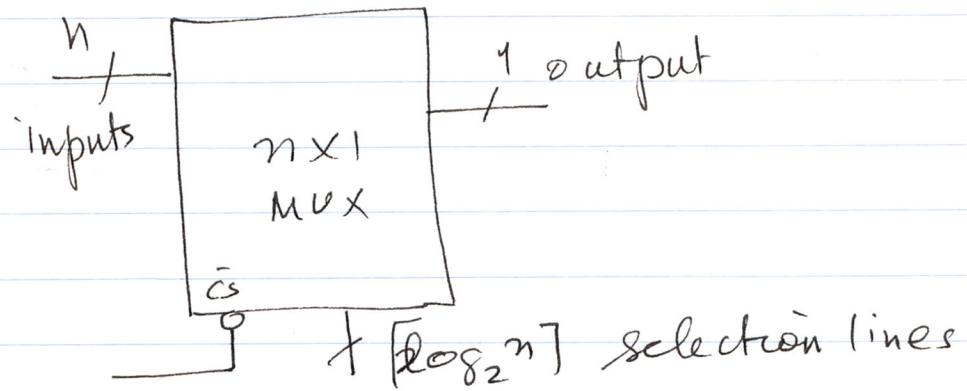

S_1	S_0	D
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

I Build larger Mux using smaller Muxs.

II Building Combinational Circuits using $n \times 1$ Muxs.

Build a 8x1 Mux using 2 4x1 Mux

