

CSE241

①

March 1, 2017

Mid Term Exam 3/13/2017

During lecture 50 min exam
we will review next week

CSE241


let office hours be pinned

Full Adder : MSI Medium Scale Integration

1-bit full adder (FA) $\approx 10 - 100$ gate complexity

4-bit FA

1. Block diagram

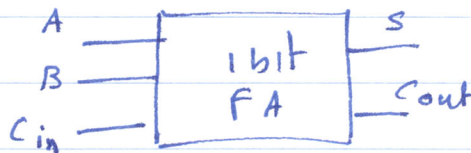

2. Truth Table outputs

	inputs			outputs	
	A	B	Cin	S	Cout
m ₀	0	0	0	0	0
m ₁	0	0	1	1	0
m ₂	0	1	0	1	0
m ₃	0	1	1	0	1
m ₄	1	0	0	1	0
m ₅	1	0	1	0	1
m ₆	1	1	0	0	1
m ₇	1	1	1	1	1

add \uparrow

$$S(A, B, C_{in}) = \sum(1, 2, 4, 7)$$

	Cin			
	00	01	11	10
0	0	1	3	2
1	4	5	7	6

$$= A'B'C_{in} + A'BC_{in}' + AB'C_{in}' + ABC_{in}$$

$$= C_{in}'(A'B + AB') + C_{in}(A'B' + AB)$$

$$= C_{in}'(A \oplus B) + C_{in}(A \odot B)$$

$$= C_{in}'(x) + C_{in}(x)'$$

$$= C_{in}'x + C_{in}x'$$


$$= C_{in} \oplus x = C_{in} \oplus (A \oplus B)$$

$$C_{in} \oplus A \oplus B \text{ (Sum)}$$

$$P \oplus Q = (P \odot Q)'$$


March 1, 2017

es (3)

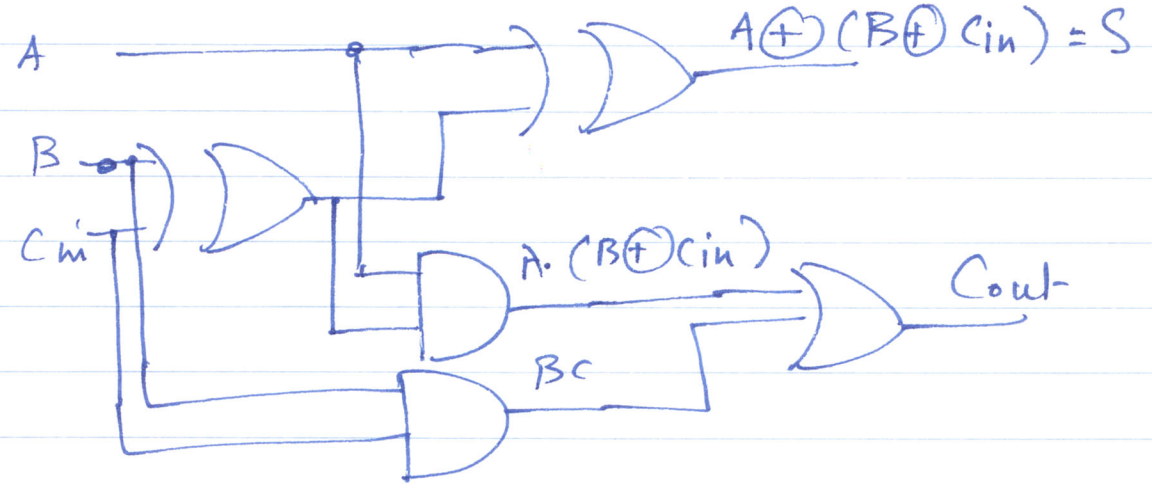


1-bit full adder (FA)

The chip is 4-bit FA IC MSI

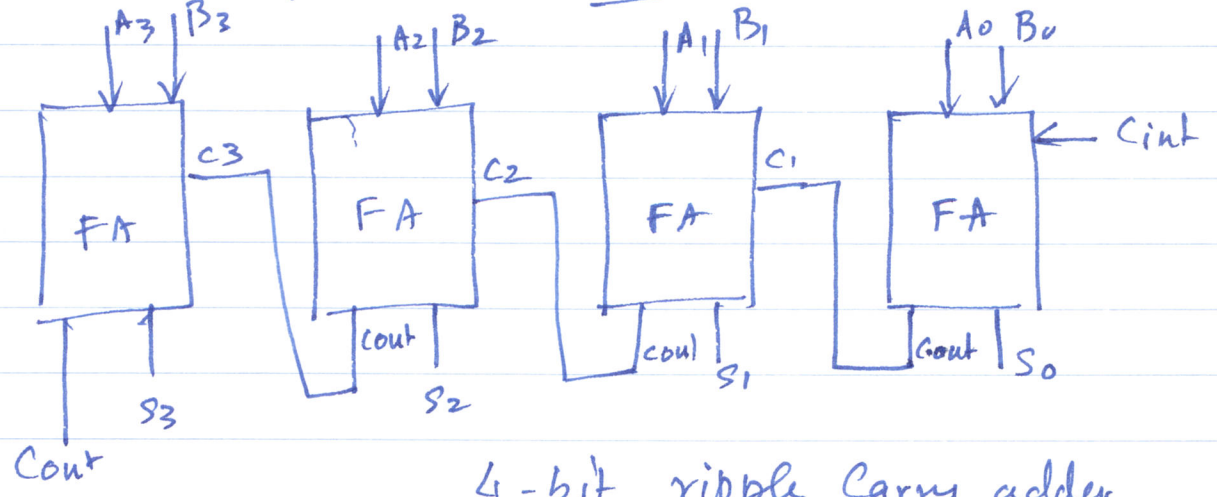


4-bit ripple carry adder

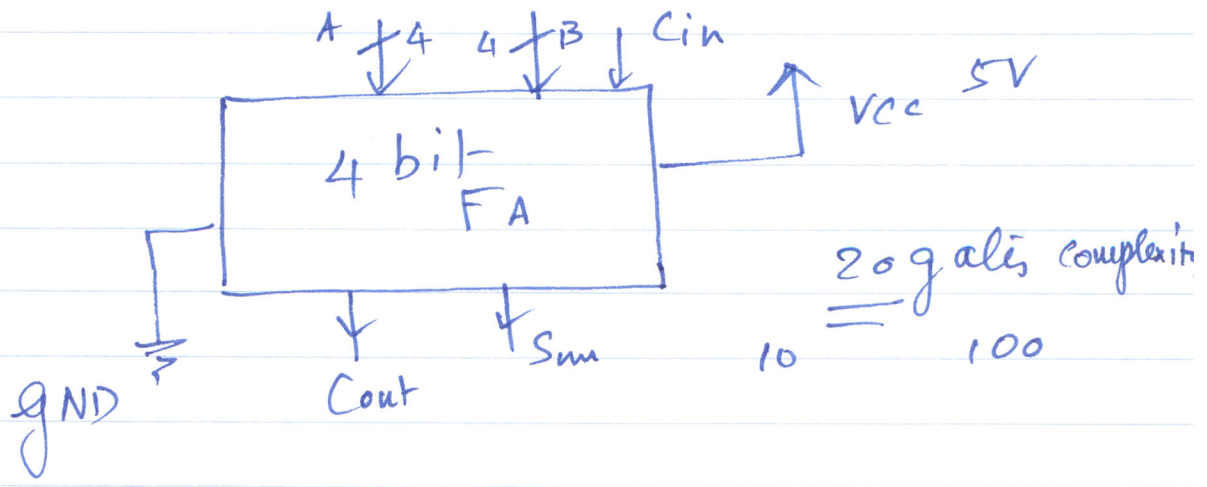

March 1, 2017

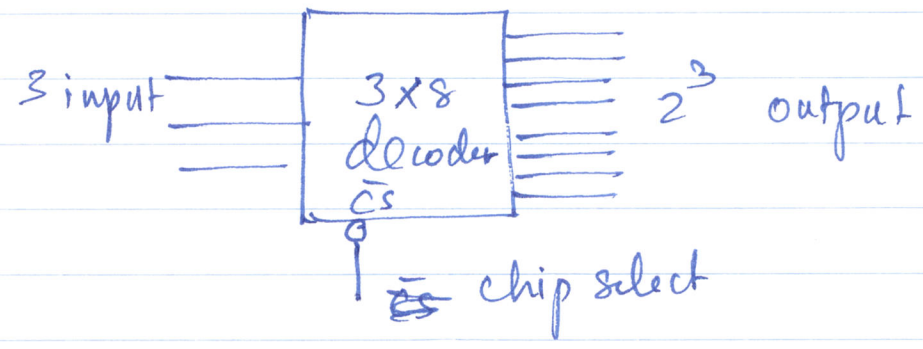Decoder: MSI chip
Motivation → address decoding is an important application



De Morgan's law: applied ()' when you have a primed term or expression

Problem $(AB + B'C)'$ transform this into a standard sum of products form.

$$(A \cdot B)' \cdot (B' + C)'$$

$$(A' + B') \cdot (B + C)$$

$$A'B + A'C + \cancel{B \cdot B} + B'C$$

$$A'B + A'C + B'C$$