

CSE 241

Feb 22, 2017

Announcements:

Midterm Exam 3/13/2017
We'll review for it before the exam.


Lab 1 is posted.

All the lecture recordings available on Ublearns

HW#2 is also assigned: look at the Homeworks Tab.

Reading: We are in ch. 3

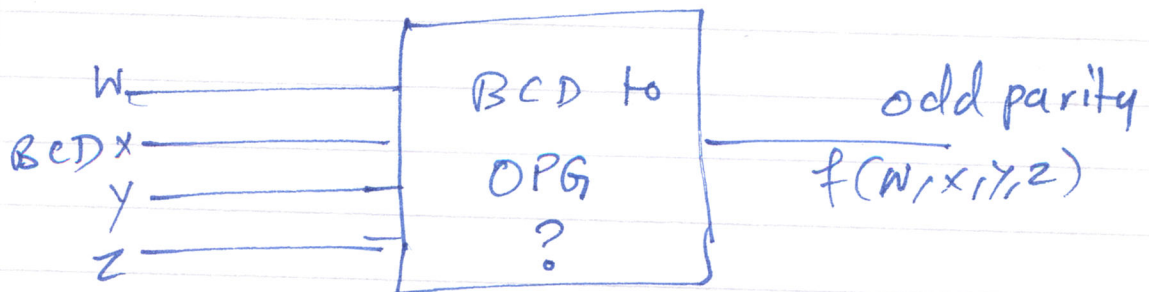BCD - Binary Coded Decimal
to - Odd Parity Generator



Combinational Circuit

Output is dependent only on the input for a given circuit

(2)

Feb 22, 2017

BCD digit	Truth Table				output
	w	x	y	z	
0	0	0	0	0	1
1	0	0	0	1	0
2	0	0	1	0	0
3	0	0	1	1	1
4	0	1	0	0	0
5	0	1	0	1	1
6	0	1	1	0	1
7	0	1	1	1	0
8	1	0	0	0	0
9	1	0	0	1	1

\Rightarrow 5 bits together
 will have odd
 # of 1's

step 1: ~~find~~ Problem
 to TT

step 2: TT \rightarrow
 Σ minterms

$f(w,x,y,z)$
 $= \Sigma (m_0, m_3, m_5, m_6, m_9)$

Other combinations
 are not needed
 since they will
 not occur in
 the input
 "don't cares"

step 3: K-map

version 1: without
 don't cares

version 2: with
 don't cares

5

Version 1

Feb 22, 2017

		yz			
		00	01	11	10
wx	00	0 1	1	3 1	2
	01	4	5 1	7	6 1
	11	12	13	15	14
	10	8	9 1	11	10

map the minterms

Standard form:

$$f(w, x, y, z) = w'x'y'z' + w'x'y'z + wx'y'z + w'x'yz' + wx'y'z + w'x.yz$$

Version 2:

$$f(w, x, y, z) = \sum (0, 3, 5, 6, 9)$$

$$d(w, x, y, z) = \sum m_{10}, m_{11}, m_{12}, m_{13}, m_{14}, m_{15}$$

$$= \sum (10, 11, 12, 13, 14, 15)$$

These terms and cells are available for simplification IF YOU WANT TO USE THEM
 You don't have to cover all of them.

		yz			
		00	01	11	10
wx	00	0 1	1	3 1	2
	01	4	5 1	7	6 1
	11	12	13	15	14
	10	8	9 1	11	10

$$w'x'y'z' + x'y'z + xy'z + x'yz' + wxyz$$

wz

↑ group of 4

(4)

Feb 22, 2017

$$f(w,x,y,z) = w'x'y'z' + x'yz + xy'z + xyz' + wz$$

Assume primes are available.

Use only NAND gates to implement this function.

Assume 5-input, 4-input, 3-input, 2-input NANDs are available

