
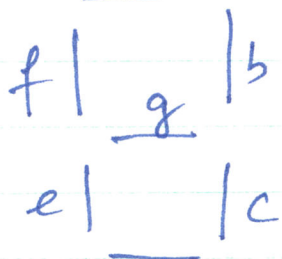


CSE241

Feb 24, 2014

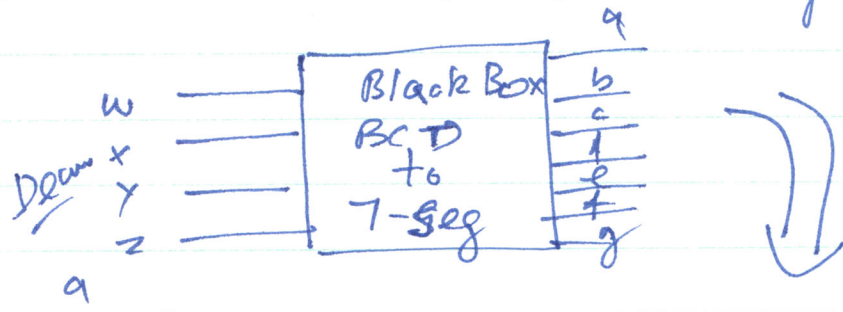Design a combinational circuit (s) that will convert BCD \rightarrow 7-segment display



Truth Table

7 output functions

BCD	"BCD" d input variables				output variables						
	w	x	y	z	a	b	c	d	e	f	g
0	0	0	0	0	1	1	1	1	1	1	0
1	0	0	0	1	0	1	1	0	0	0	0
2	0	0	1	0	1	1	0	1	1	0	1
3	0	0	1	1	1	1	1	1	0	0	1
4	0	1	0	0	0	1	1	0	0	1	1
5	0	1	0	1	1	0	1	1	0	1	1
6	0	1	1	0	1	0	1	1	1	1	1
7	0	1	1	1	1	1	1	0	0	0	0
8	1	0	0	0	1	1	1	1	1	1	1
9	1	0	0	1	1	1	1	0	0	1	1

Simplify using K-maps, expressions for a, b, c, d, e, f, g. Use don't cares.

Feb 24, 2014

$a = ?$ $a(w, x, y, z) = ?$

w \ x \ y \ z	00	01	11	10
00	0	1	1	1
01	0	1	1	1
11	d	d	d	d
10	0	1	1	1

$a = \Sigma(0, 2, 3, 5, 6, 7, 8, 9)$

don't care

$10, 11, 12, 13, 14, 15$


term 1 = y

term 2 = w

term 3 = xz

term 4 = $x'z'$

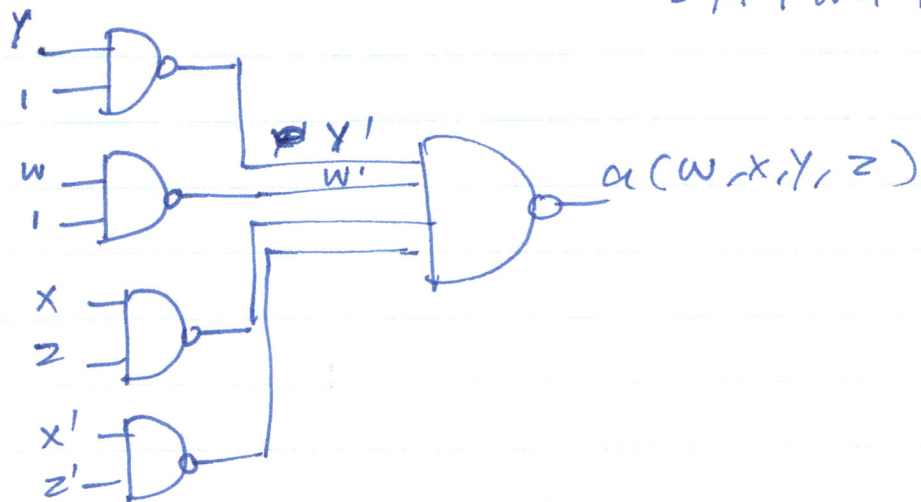$a(w, x, y, z) = y + w + xz + x'z'$
 $= y \cdot 1 + w \cdot 1 + xz + x'z'$




3

Feb 24, 2017

$b(w, x, y, z) = \Sigma (0, 1, 2, 3, 4, 7, 8, 9)$


don't cares: 10, 11, 12, 13, 14, 15

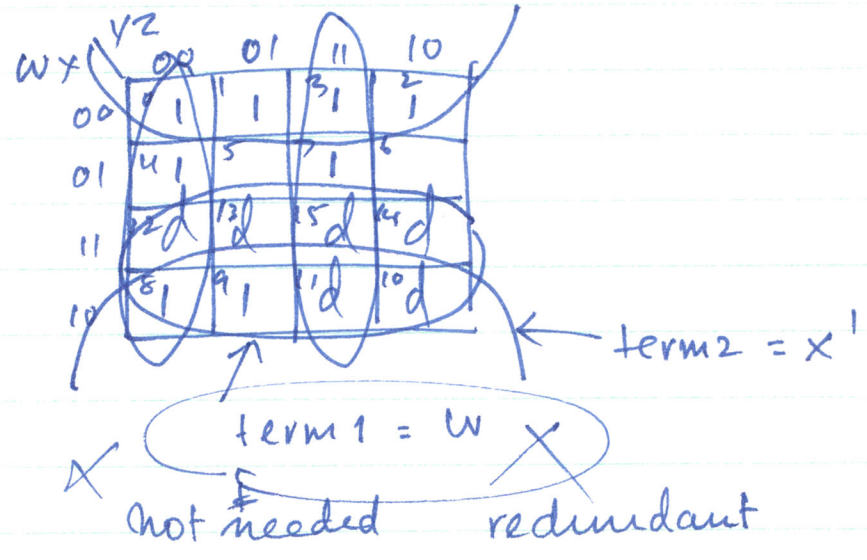our goal is to cover the 1's using minimal # of groups.



term 3 = $y'z'$ term 4 = yz

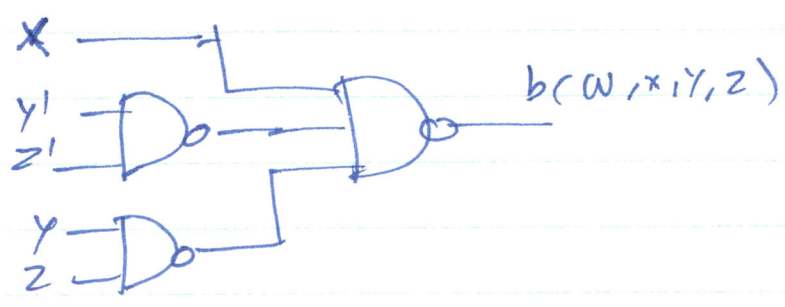$b(w, x, y, z) = w + x' + y'z' + yz$
 ↑
 (-)
 $= x' + y'z' + yz$




$e(w, x, y, z) = \sum (0, 2, 6, 8)$
 don't care 10, 11, 12, 13, 14, 15

	yz 00	01	11	10
wx 00	0	1	3	2
01	4	5	7	6
11	12	13	15	14
10	8	9	11	10

term 1 $\rightarrow x'z' + yz'$
 $= z'(x' + y)$

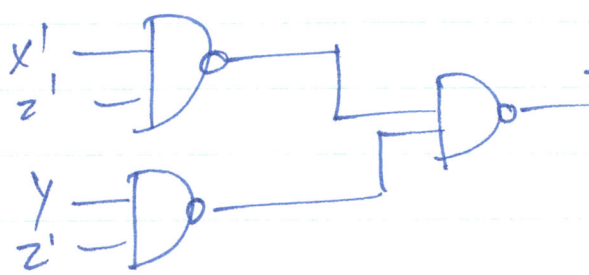Standard form that can be easily implemented using only NAND gate



a, b, e

c, d, f, g