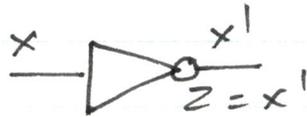


Logic gates 1. name 2. graphic symbol
3. algebraic symbol 4. logic expression 5. Truth Table


I Inverter

NOT



input	output
x	z
0	1
1	0


II Buffer

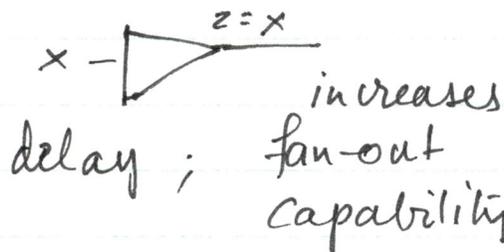

input	output
x	z
0	0
1	1

"boost"


III

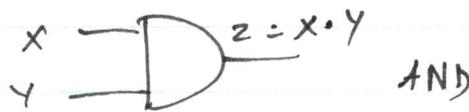

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

$z = x \cdot y = xy$

IV

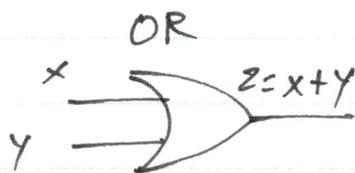

x	y	z
0	0	0
0	1	1
1	0	1
1	1	1


V



x	y	z
0	0	0
0	1	1
1	0	1
1	1	0


$z = x \oplus y$
 $= x' \cdot y + x \cdot y'$

Feb 13, 2017 (C)

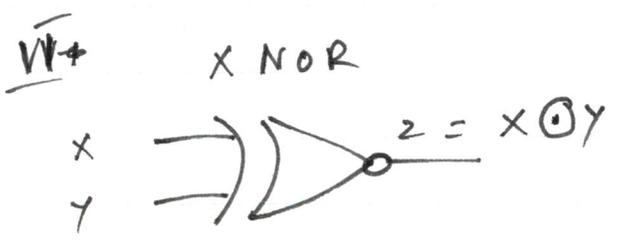


input		output
x	y	z
0	0	1
0	1	0
1	0	0
1	1	1

$z = x \odot y$
 $= x'y' + x'y$

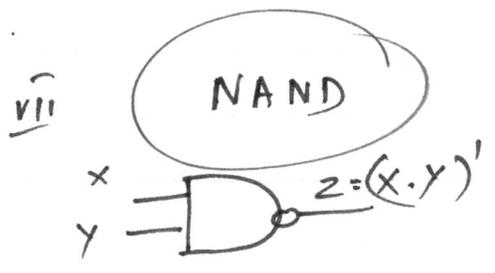

x	y	z
0	0	1
0	1	1
1	0	1
1	1	0

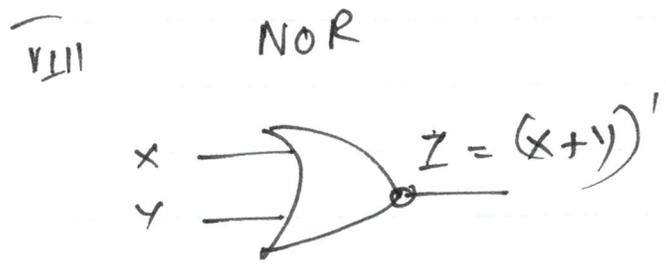$z = (x \cdot y)'$
 $= x' + y'$
DeMorgan's law



input		output
x	y	z
0	0	1
0	1	0
1	0	0
1	1	0

$z = (x + y)'$
 $= x' \cdot y'$


Problem $F(A, B, C) = \sum (1, 4, 5, 6, 7)$
Given this function, simplify to minimum # of terms + literals. Use algebraic simplification

$$\begin{aligned}
 & \overset{1}{A'B'C} + \overset{4}{ABC'} + \overset{5}{AB'C} + \overset{6}{ABC'} + \overset{7}{ABC} \\
 & \overset{001}{A'B'C} + \overset{100}{ABC'} + \overset{101}{AB'C} + \overset{110}{ABC'} + \overset{111}{ABC} \\
 & = A'B'C + AB'(C'+C) + AB(C'+C) \\
 & = A'B'C + AB' + AB = A'B'C + A(B'+B) \\
 & = A' \cdot B'C + A = (A'+A) \cdot (B'C+A) \\
 & = \underline{\underline{B'C + A}}
 \end{aligned}$$

Assess: Simplification ↓ 5 15
2 terms 3 literals

Feb 13, 2017

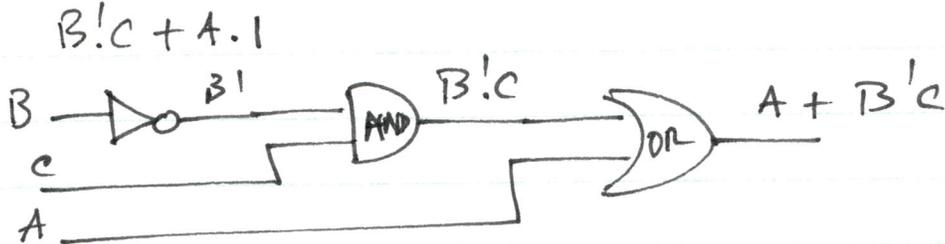Implement the simplified expression using (i) { NOT, AND, OR } (ii) only NAND



Three diff. types of gates:

NOT	hex inverter	74LS06	NOT or inverter IC
AND	quad AND	74LS08	AND IC
OR	quad OR	74LS32	AND OR IC


inventory

NAND implementation.

Implement each term with NAND gate
Sum up the terms (output of NAND) using another NAND gate.

$f(A, B, c) = B'c + A \cdot 1$

assume B' is available.

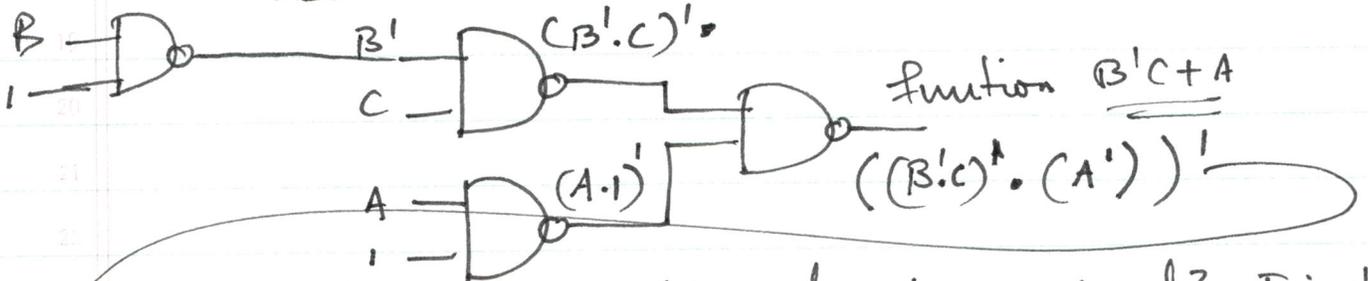

what IC chip do you need? I just need only 1 kind. NAND IC

quad NAND

74LS00

$((B'c)' \cdot A')' = (B'c) + A = B'c + A$

DeMorgan's law; Proceed equivalent

Feb 13, 2018


If the final simplified function is in sum of products form: how do you implement it using only NAND gates?

step 1: Implement each term using a NAND

step 2: sum all the NAND outputs in step 1 using another NAND gate.

$$F(x, y, z) = x'y + xy' + x'y'z'$$

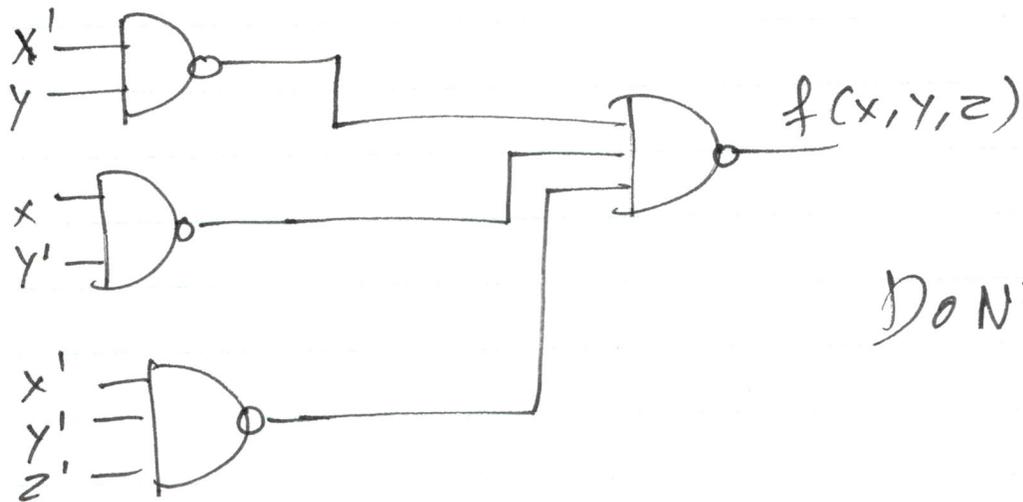Assumes: Prime of variables are available
3-input NAND gate is available



DONE