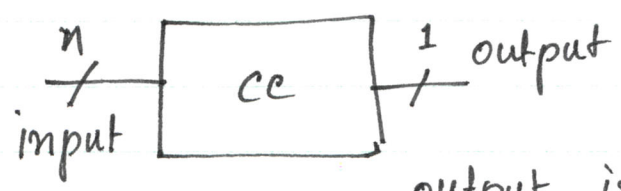


1. combinational circuit (cc)



output is dependent only on the inputs for a given cc

2. BCD

Binary Coded Decimal

4 bit binary representing a decimal digit

decimal digit

{ 0, 1, 2, 3, 4, 5, 6, 7, 8, 9 }

3. Find the odd parity for the BCD input



4. What is parity? parity bit? odd parity bit?

5. Truth Table

② Feb 10, 2017

"BCD"	Truth Table odd				p	
	w	x	y	z		
0	0	0	0	0	1	m ₀
1	0	0	0	1	0	m ₁
2	0	0	1	0	0	m ₂
3	0	0	1	1	1	m ₃
4	0	1	0	0	0	m ₄
5	0	1	0	1	1	m ₅
6	0	1	1	0	1	m ₆
7	0	1	1	1	0	m ₇
8	1	0	0	0	0	m ₈
9	1	0	0	1	1	m ₉

write the Boolean expression.

$$f(w, x, y, z) = \sum (m_0, m_3, m_5, m_6, m_9)$$

$$= w'x'y'z' + w'x'yz + w'xy'z + w'xyz' + wx'y'z$$

simplify this.

Other combinations of 1's, 0's do not occur in the input

5 terms \downarrow $5 \times 4 = 20$ literals

Goal of simplification:

Minimize # of terms

Minimize # of literals

$$f(w, x, y, z) = \underline{w'x'y'z'} + \underline{w'x'yz} + \underline{w'xy'z} + \underline{w'xyz'} + \underline{wx'y'z}$$

$$= w'x'(y'z' + yz) + w'x(y'z + yz') + wx'y'z$$

$$\rightarrow w'x'y'z' + w'x'yz + w'y'z(x + x') + w'xyz'$$

$$= w'x'y'z' + w'z(x' + y') + w'xyz'$$

$$= w'x'y'z' + w'z((x' + y')(y + y')) + w'xyz'$$

$$w'x'(y'z' + yz) + w'x(y'z + yz') + wx'y'z$$


$$w'x' \cdot (y \oplus z)' + w'x \cdot (y \oplus z) + wx'y'z$$

We'll repeat this with K-map & don't care's

Feb 10, 2017 (3)

Implement.

$$f(w,x,y,z) = w'x'(y \oplus z)' + w'x.(y \oplus z) + wx'y'z$$

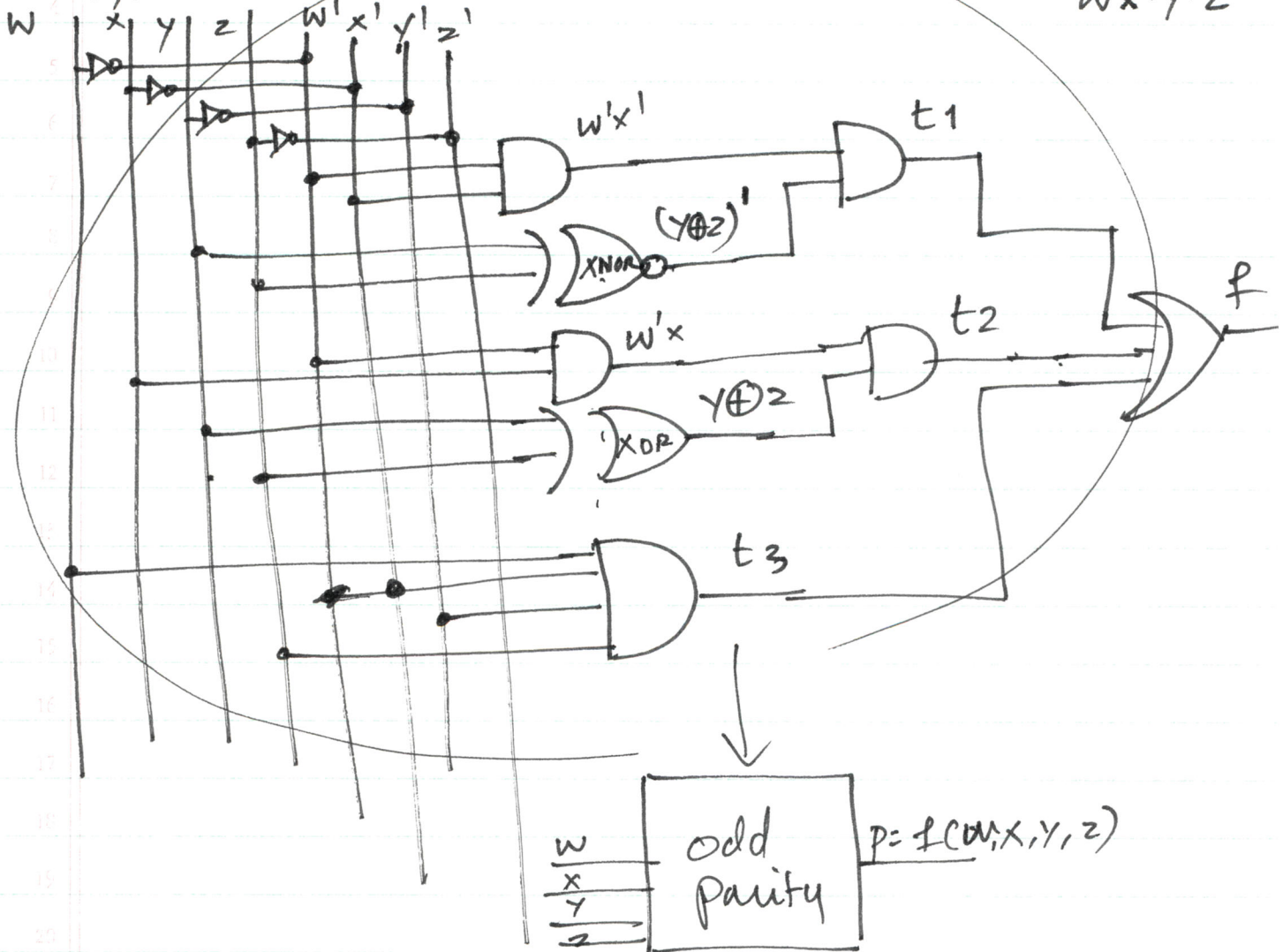

Lab 1: SAND, OR, NOT & gates to implement logic expressions.

"NAND" gate

$$f(a, b, c) = \cancel{a'bc} + \cancel{ac} = a'b + ac + cb$$

Implement this using (i) { AND, OR, NOT }
(ii) NAND only

What is NAND?

X	Y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

X	Y	AND
0	0	0
0	1	0
1	0	0
1	1	1

