

CSE241

March 6
Spring 2017


3/8 : Exam 1 Review

3/10 : 30 min Exam 1 Review


3/13 : Exam 1

3/15 : Lab 2 in-class explanation

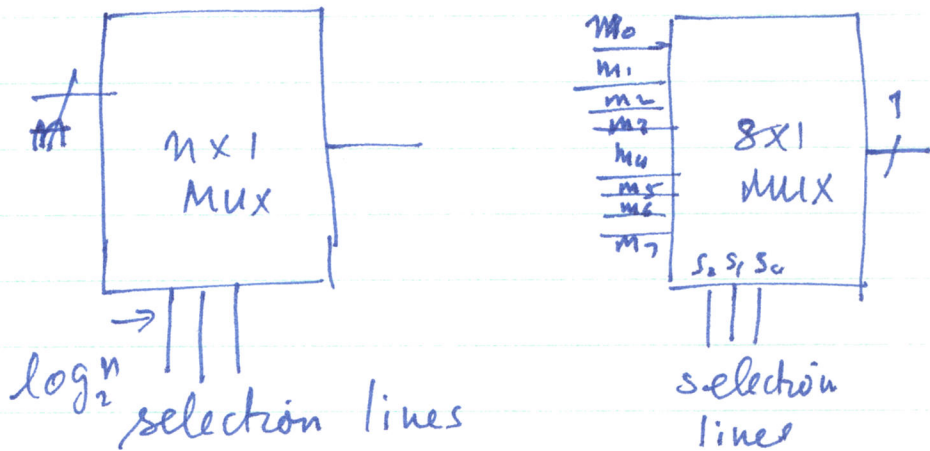Building Combinational Circuits using a Mux.


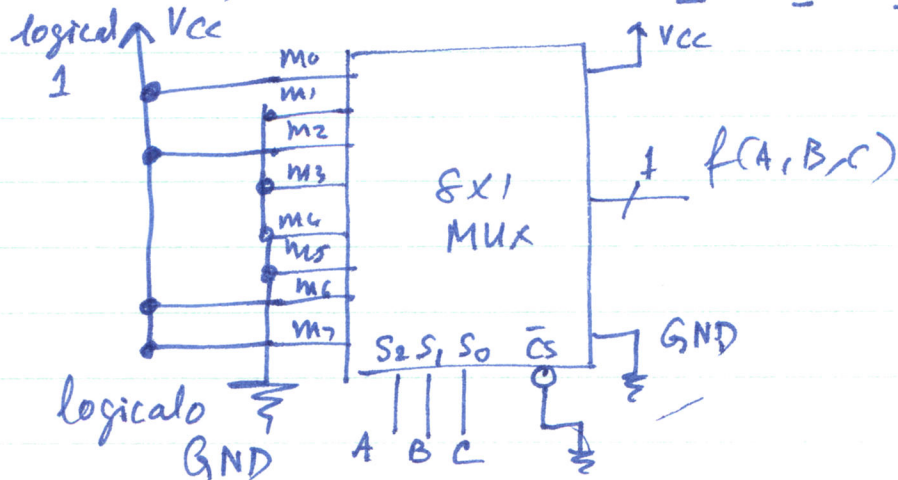
$$f(A, B, C) = \sum (m_0, m_2, m_6, m_7)$$




Implement a combinational circuit using 4x1 Mux.

(i) $f(A, B, C) = \sum (m_0, m_2, m_6, m_7)$

(ii) $f(W, X, Y, Z) = \sum (m_0, m_1, m_2, m_7, m_{15})$

(i)

	A	B	C	$f(A, B, C)$	
m_0	0	0	0	1	$I_0 = C'$
m_1	0	0	1	0	
m_2	0	1	0	1	$I_1 = C'$
m_3	0	1	1	0	
m_4	1	0	0	0	$I_2 = 0$
m_5	1	0	1	0	
m_6	1	1	0	1	
m_7	1	1	1	1	$I_3 = 1$

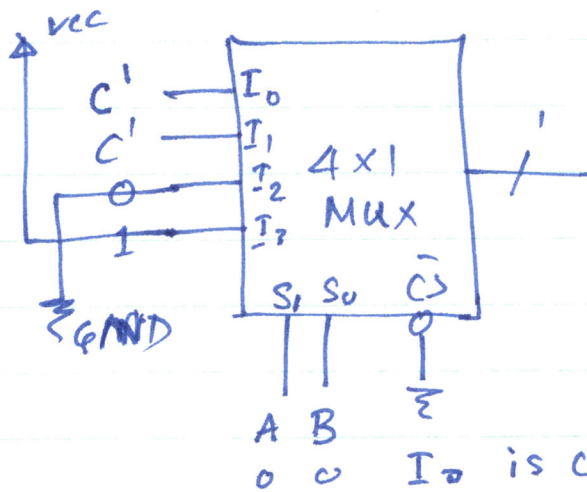

- 0 0 I_0 is connected to the output
- 0 1 I_1 is connected to the output
- 1 0 I_2 is connected to the output
- 1 1 I_3 is connected to the output

March 6, 2017
 (3)

(ii)

$f(w, x, y, z) = \sum (m_0, m_1, m_2, m_7, m_{15})$
 "given"


	w	x	y	z	$f(w, x, y, z)$
I_0	0	0	0	0	1
	0	0	0	1	1
	0	0	1	0	1
	0	0	1	1	0
I_1	0	1	0	0	0
	0	1	0	1	0
	0	1	1	1	1
I_2	1	0	0	0	0
	1	0	0	1	0
	1	0	1	0	0
I_3	1	0	1	1	0
	1	1	0	0	0
	1	1	0	1	0
	1	1	1	1	1

~~$f(w, x, y, z) =$~~
 NAND $I_0 = (y \cdot z)'$

AND $I_1 = y \cdot z$

$I_2 = 0$

$I_3 = y \cdot z$

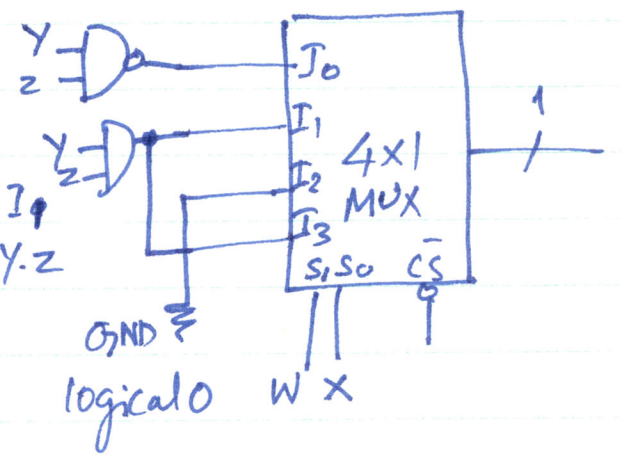

$f_1(w, x, y, z) = \sum (m_0, m_1, m_2, m_7, m_{12}, m_{15})$

y	z	$f(w, x, y, z)$
0	0	1
0	1	0
1	0	0
1	1	1

$I_2 = (y \oplus z)'$
 $= (y \odot z)$

1
2
3
4
5
6
7
8
9
10
11
12
13
14
15
16
17
18
19
20
21
22
23
24
25
26
27
28

$$\begin{array}{c|c|c}
 Y & z & f(w, x, z) \\
 \hline
 0 & 0 & 1 \\
 0 & 1 & 1 \\
 1 & 0 & 0 \\
 1 & 1 & 0
 \end{array}$$

I_3

~~f~~ ~~$f(w, x)$~~

$$\begin{aligned}
 I_3 ? &= Y'z' + Y'z \\
 &= Y'(z' + z) \\
 &= \quad \quad \quad \leftarrow 1
 \end{aligned}$$