

Boolean algebra

B. Algebraic simplification

1. literals x, y, A, B
 single x' A'

constants $\{0, 1\}$ binary

bit arithmetic

	cin	s	cout
$0 + 0 + 0$	0	0	0
$0 + 0 + 1$	1	0	0
$0 + 1 + 0$	1	0	0
$0 + 1 + 1$	0	1	1
$1 + 0 + 0$	1	0	0
$1 + 0 + 1$	0	1	1
$1 + 1 + 0$	0	1	1
$1 + 1 + 1$	1	1	1

2. Terms Boolean algebraic terms

need operators

Boolean operators

$\{+, \cdot, '\}$

$\{OR, AND, NOT\}$

$f(x, y, z)$

$x \cdot y \cdot z$
 (xyz)

product term ✓

$(x + y + z)$

sum term (dual)

3. you use terms to make expressions
 functions are defined by expressions

$$f(x, y, z) = \underset{\substack{\uparrow \\ \text{AND}}}{x \cdot y \cdot z} + \underset{\substack{\uparrow \\ \text{OR}}}{x' \cdot y' \cdot z} = xy z + x' y' z$$

Feb 8, 2017 (2)

4. Product terms

$f(x, y)$		$f(x, y, z)$
x	y	
0	0	$x'y'$
0	1	$x'y$
1	0	xy'
1	1	xy

2 variable product terms


$f(x, y, z)$ Truth table: versatile tool

Minterm	x	y	z	product terms
m_0	0	0	0	$x'y'z'$
m_1	0	0	1	$x'y'z$
m_2	0	1	0	$x'yz'$
m_3	0	1	1	$x'yz$
m_4	1	0	0	$xy'z'$
m_5	1	0	1	$xy'z$
m_6	1	1	0	xyz'
m_7	1	1	1	xyz

3 ^{0,1} $2^3 = 8$
Product terms

Complete product terms
"minterms"

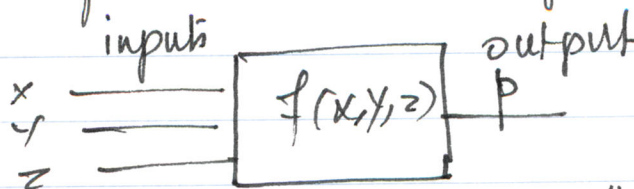5. function(s): A function takes n inputs, performs Boolean operations of n inputs, and produces an output. "Block diagram"



Express the function using "sum" of minterms

$$f_2(x, y, z) = x'y'z + x'yz + xy'z + xy'z'$$

$$= \sum (1, 3, 4, 5) = m_1 + m_3 + m_5 + m_4$$

Feb 8, 2017 (3)

6. Implement the function

$$f_2(x, y, z) = x'y'z + x'yz + xy'z + xy'z'$$


AND OR NOT

We need logic gates

6a. Logic gate:

1. name of the gate
2. graphic system
3. algebraic symbol
4. algebraic expression
5. Truth table explaining its operation



1. AND.

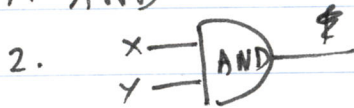

4. $X \cdot Y$

5.

X	Y	X.Y
0	0	0
0	1	0
1	0	0
1	1	1

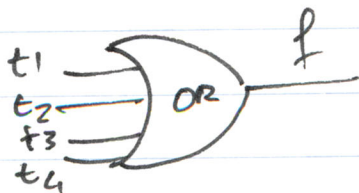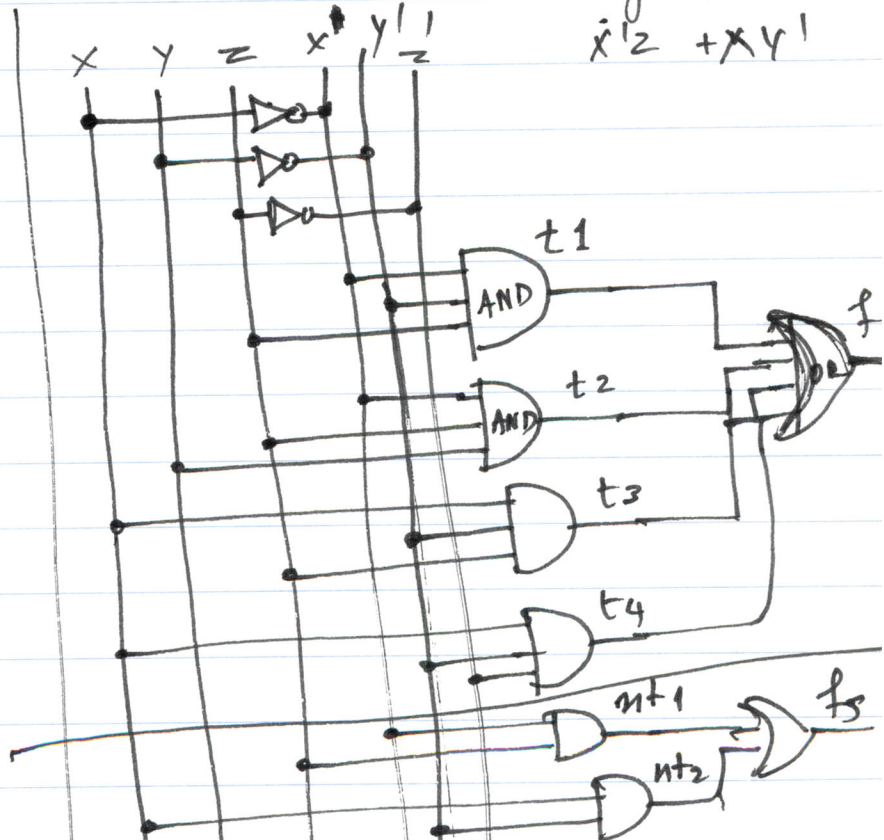

7. Simplification:

goal of simplification:

1. ~~reduce~~ Reduce the number of terms.
2. Reduce the # of literals / term \Rightarrow less gates

Minimization

(4)

Feb 8, 2017

$$f_2(x, y, z) \equiv \underline{x'y'z} + \underline{x'yz} + \underline{xy'z} + \underline{xy'z'}$$

Simplify this to minimum number of terms of literals.

use ~~the~~ Boolean algebra.

$$\begin{aligned} & x'(y'z + yz) + x(y'z + y'z') \\ &= x'(\underbrace{y' + y}_{\downarrow 1}) + x(y'(\underbrace{z + z'}_{\downarrow 1})) \end{aligned}$$

$$= x'(z \cdot 1) + x(y' \cdot 1)$$

$$= x'z + xy'$$

We went from 4 terms of 3 literals each to 2 terms

each term has only 2 literals now

from $4 \times 3 = 12$ literals $\Rightarrow 2 \times 2 \Rightarrow 4$ literal

$$12 \rightarrow 4$$

lets implement this!