

adder.v

April 12, 2017

①

http://www.cse.buffalo.edu/~bina/cse241/spring2017/verilog/adder.v


```

module ex2_1;
  /* gate level model to implement an adder */

  wire [3:0] sum, inA, inB;
  wire      carry;

  adder4 a4 (sum, carry, inA, inB);
  adderTest at (inA, inB, sum, carry);
endmodule

```

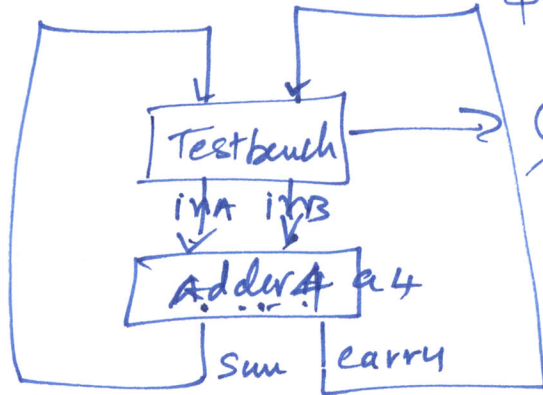

\$monitor
Run
⊙

```

module adder4 (sum, carry, inA, inB);
  output [3:0] sum;
  output carry;
  input [3:0] inA, inB;

  adder1 a0 (sum[0], c0, inA[0], inB[0], 1'b0);
  adder1 a1 (sum[1], c1, inA[1], inB[1], c0);
  adder1 a2 (sum[2], c2, inA[2], inB[2], c1);
  adder1 a3 (sum[3], carry, inA[3], inB[3], c2);
endmodule

```


1-bit full adder description

```

module adder1 (s, cout, a, b, cin);
  output s, cout;
  input a, b, cin;

  xor (t1, a, b);
  xor (s, t1, cin);
  and (t2, t1, cin);
  and (t3, a, b);
  or (cout, t2, t3);
endmodule

```

 

①
⑤

```

module adderTest (A, B, sum, carry);
  output [3:0] A, B;
  input [3:0] sum;
  input carry;
  reg [3:0] A, B;

```



integer i, j; // loop variables

```

initial begin
  $monitor ("A: %d B: %d sum: %d carry: %d", A, B, sum, carry);
  $dumpfile("adder_wv.vcd");
  $dumpvars(1, A, B, sum, carry);

  for (i=0; i<16; i=i+1) for (j=0; j<16; j=j+1)
    begin A=i; B=j; #10000; end
  $finish;
end
endmodule

```

\$ directive

\$dumpvars;

print
format
string
Based on c
lang

`adder4` `adderTest`

Ripple carry adder


```

module ex2_1;
  /* gate level model to implement an adder */

  wire [3:0] sum, inA, inB;
  wire      carry;

  ? → adder4 a4 (sum, carry, inA, inB);
  adderTest at (inA, inB, sum, carry);
endmodule
    
```

output input

 

```

module adder4 (sum, carry, inA, inB);
  output [3:0] sum;
  output carry;
  input [3:0] inA, inB;

  .adder1 a0 (sum[0], c0, inA[0], inB[0], 1'b0);
  .adder1 a1 (sum[1], c1, inA[1], inB[1], c0);
  .adder1 a2 (sum[2], c2, inA[2], inB[2], c1);
  .adder1 a3 (sum[3], carry, inA[3], inB[3], c2);
endmodule
    
```


```

(1) module adder1 (s, cout, a, b, cin);
(2)   output s, cout;
      input a, b, cin;
    
```

"scale up" Structural Verilog

```

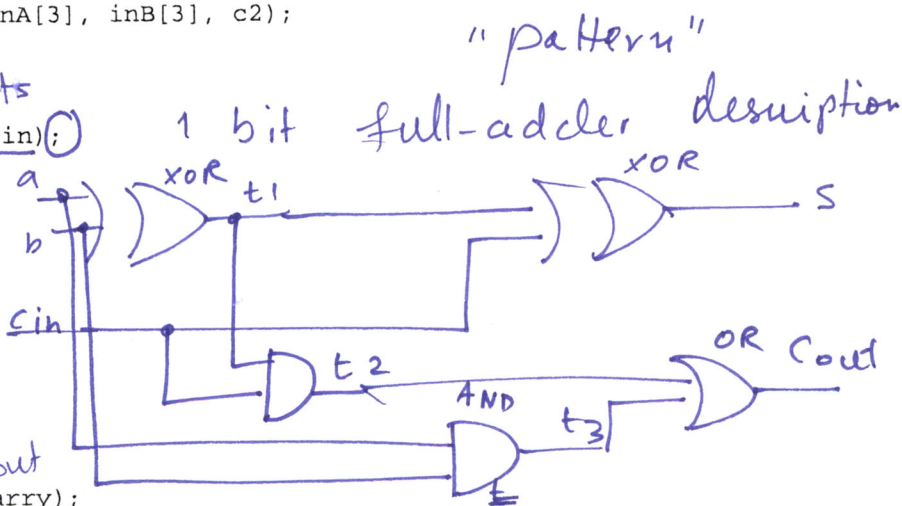xor (t1, a, b);
xor (s, t1, cin);
and (t2, t1, cin);
and (t3, a, b);
or (cout, t2, t3);
endmodule
    
```



```

module adderTest (A, B, sum, carry);
  output [3:0] A, B;
  input [3:0] sum;
  input carry;
  reg [3:0] A, B;
    
```

// place holder for the test patterns


```

integer i, j; // loop variables
initial begin
  $monitor ("A: %d B: %d sum: %d carry: %d", A, B, sum, carry); ← directive
  $dumpfile("adder_wv.vcd"); ← directive
  $dumpvars(1, A, B, sum, carry); ← directive
  ( for (i=0; i<16; i=i+1) for (j=0; j<16; j=j+1)
    begin A=i; B=j; #10000; end
  $finish;
end
endmodule
    
```

simulation



%.d decimal format

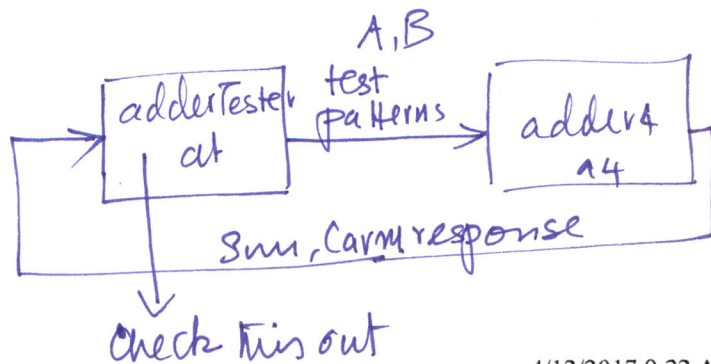

```
module ex2_1;
    /* gate level model to implement an adder */

    wire [3:0] sum, inA, inB;
    wire      carry;

    adder4 a4 (sum, carry, inA, inB);
    adderTest at (inA, inB, sum, carry);
endmodule

module adder4 (sum, carry, inA, inB);
    output [3:0] sum;
    output carry;
    input [3:0] inA, inB;

    adder1 a0 (sum[0], c0, inA[0], inB[0], 1'b0);
    adder1 a1 (sum[1], c1, inA[1], inB[1], c0);
    adder1 a2 (sum[2], c2, inA[2], inB[2], c1);
    adder1 a3 (sum[3], carry, inA[3], inB[3], c2);
endmodule

module adder1 (s, cout, a, b, cin);
    output s, cout;
    input a, b, cin;

    xor (t1, a, b);
    xor (s, t1, cin);
    and (t2, t1, cin),
        (t3, a, b);
    or (cout, t2, t3);
endmodule

module adderTest (A, B, sum, carry);
    output [3:0] A, B;
    input [3:0] sum;
    input carry;
    reg [3:0] A, B;

    integer i, j;
    initial begin
        $monitor ("A: %d B: %d sum: %d carry: %d", A, B, sum, carry);
        $dumpfile("adder_wv.vcd");
        $dumpvars(1, A,B, sum, carry);

        for (i=0; i<16; i=i+1) for (j=0; j<16; j=j+1)
            begin A=i; B=j; #10000 ;end
        $finish;
    end
endmodule
```