 



1. [10 pts] Implement the given logic function using Complementary CMOS Logic.

$$f = \neg[(A.B + C.D).E] \Rightarrow PDN$$


$$f = (\bar{A} + \bar{B}) \cdot (\bar{C} + \bar{D}) + \bar{E} \Rightarrow PUN$$



 2. (8 points) Design a 2:1 Multiplexer using CMOS Transmission Gate Logic. Consider inputs A, B; Select line: S; Output: Out



 3. (10 points) Voltage Transfer Characteristics of an inverter is given in Fig 1. Determine V_{IL} , V_{OL} , V_{IH} , V_{OH} , N_{ML} and N_{MH} . Show the steps



$$V_{IL} = 1V$$

$$V_{IH} = 1.5V$$

$$V_{OL} = 0V$$

$$V_{OH} = 2.5V$$

$$N_{ML} = V_{IL} - V_{OL} = 1V - 0V$$

$$N_{MH} = V_{OH} - V_{IH} = 2.5V - 1.5V$$

Fig. 1

4. (10 points) Input and output waveforms of a CMOS inverter are given in Fig. 2.


(a) Calculate the propagation delay (t_p) of the inverter (Hint: Calculate t_{pHL} and t_{pLH}); Show the steps

$$t_{pLH} = 11 - 9 = 2$$

$$t_{pHL} = 5 - 3 = 2$$

$$t_p = \frac{2+2}{2} = 2$$

(b) Calculate rise time and fall time

 

$$t_R = 12 - 10 = 2$$

$$t_F = 5.5 - 4.5 = 1$$


Fig. 2

5. [12 points]

(a) What is the logic function implemented by the static CMOS circuit shown in Fig 3(a)?

(b) Size the NMOS and PMOS devices for Performance (mark transistor size in Fig 3 (b)).

 (c) Additionally, size the NMOS and PMOS devices for symmetric rise and fall times (mark transistor sizes in Fig 3 (c)).



$$F = (A+B)(CD+E)$$

Fig. 3