
 


CSE 493/593 Homework 2 Fall 2025

 1. Determine the logic function implemented by
 - i.




- ii.



2. Answer the following:

 
- i. What's difference in the function between a D latch and a D flip-flop?
 - ii. Complete the timing diagrams for a positive-level-sensitive D latch and a positive-edge-triggered D flip-flop



Latch Q

Flipflop Q

 3. Consider the circuit in Fig. below. What is the logic function implemented by this circuit?



CSE 493/593 Homework 2 Fall 2025

4. How can you manipulate threshold voltage using body-biasing?
5. In order to drive a large capacitance ($C_L = 20 \text{ pF}$) from a minimum size gate (with input capacitance $C_i = 10 \text{ fF}$), you decide to introduce a three-staged buffer. Assume that the propagation delay of a minimum size inverter is 70 ps . Also assume that the input capacitance of a gate is proportional to its size.

(Hint: Sizing factor $f = \sqrt[N]{C_L/C_{g,1}} = \sqrt[N]{F}$;

Minimum delay through the chain $t_p = Nt_{p0}(1 + \sqrt[N]{F}/\gamma)$

- Determine the sizing of the three additional buffer stages that will minimize the propagation delay.
 - If you could add any number of stages to achieve the minimum delay, how many stages would you insert? What is the propagation delay in this case? Consider $\gamma=1$.
6. Implement the given logic function using Complementary CMOS logic. (Transistor level diagram). $F = \neg[(A+B)C+D]EF$
- Size all the transistors for
- Performance
 - Symmetric rise and fall times