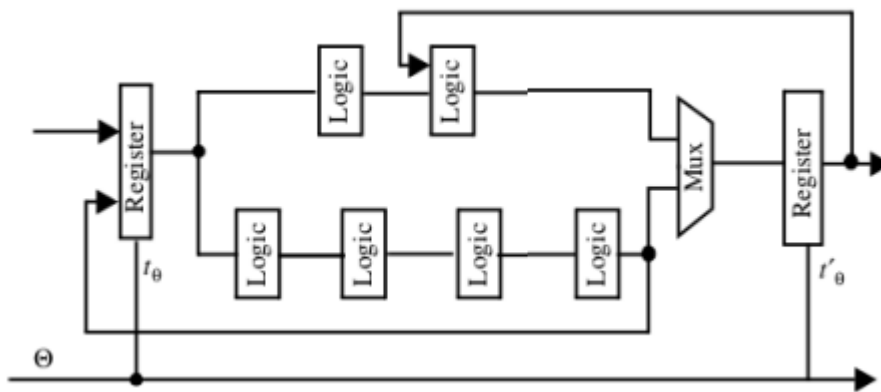



CSE 493/593 FALL 2024 HOMEWORK 5

1.
 - a. Explain how Dynamic Frequency Scaling can achieve low power.
 - b. Explain how Dynamic Voltage Scaling can achieve low power.
2. What is adaptive body biasing (ABB) technique? Describe how a designer can use this technique in low power design.
3. For the circuit shown below, assume a unit delay through the register, multiplexer and logic blocks. Assume that the registers, which are positive-edge triggered, have a unit setup time.



Determine minimum clock period disregarding clock skew.
 (Hint: $T \geq t_{c-q} + t_{logic} + t_{su}$)

 4. Given a typical memory hierarchy as shown below, list them in increasing order of
 - a. Speed
 - b. Cost per unit memory
 - c. Size



5. Draw the schematic of 6T SRAM and explain its working.