

FPGA and Verilog

Safwan Wshah Project TA

srwshah@buffalo.edu

Office hours :

- Tuesday 11-12
- Friday 12-1

Office Location: 30 Commons -- CEDAR

Semester Plan

- Week 2 – Introduction to FPGA and Verilog
- Week 3 – Structural Verilog + The Verilog HDL Test Fixture
- Week 4 – Behavioral Modeling
- Week 5 –Example
 - » Writing Modular Code in Verilog
 - » *Managing a Large Project*;
 - » I/O on the Basys 2 Board
- Week 6- Project 1 specification and grading criteria

Projects


- Project 1
 - Will be basic project that make things easy to start the final project.
- Project 2
 - Advanced project, there are many suggested projects and you can come up with your own.

FPGA

- **Field-Programmable Gate Arrays (FPGAs)** are pre-fabricated silicon devices that can be electrically programmed to become almost any kind of digital circuit or system.
- Applications of FPGAs include
 - » [digital signal processing](#),
 - » [software-defined radio](#),
 - » [Aerospace](#)
 - » [medical imaging](#), [computer vision](#),
 - » [speech recognition](#),
 - » [cryptography](#), [bioinformatics](#), [computer hardware emulation](#), [radio astronomy](#), metal detection and a growing range of other areas.


In the Final Project you will have many project options or you can come up with your own


FPGA

 



- We are going to use Basys 2 FPGA from Xilinx
 - <http://www.xilinx.com/>

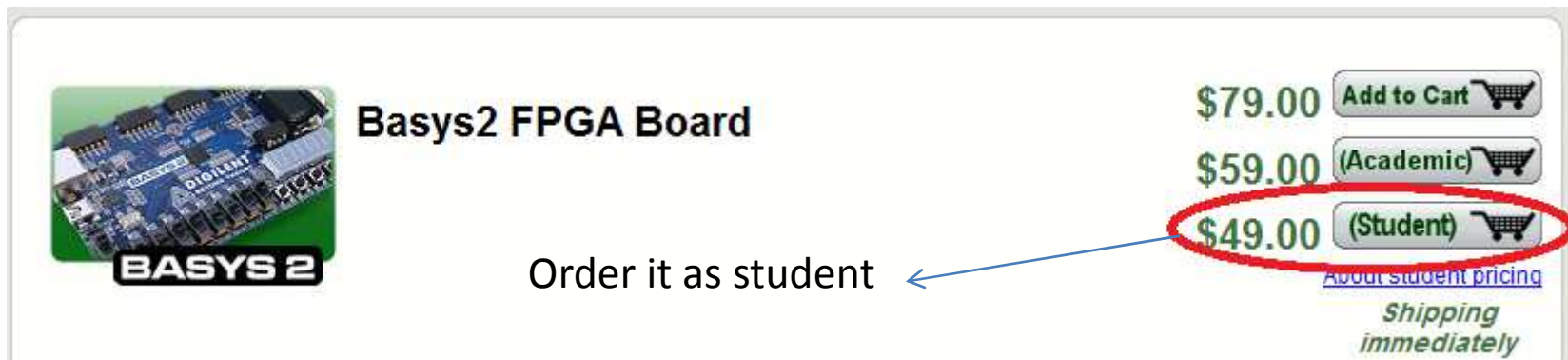
- Each student should buy his own board
 - When to buy ? **NOW**
 - How to buy?
 - Go to xilinx website , and order it from there
<http://www.digilentinc.com/Products/Detail.cfm?Prod=BASYS2>



 **Basys2 FPGA Board**

\$79.00 

\$59.00 

\$49.00 

[About student pricing](#)

Shipping immediately

Order it as student ←

Overview of Hardware Description Languages

Hardware Description Languages (HDL):

- Verilog (What we are going to use)
 - Similar syntax to C
 - Commonly used in Industry (USA & Japan)
- VHDL (VHSIC hardware description language)
 - Similar syntax to ADA(extended from Pascal)
 - Commonly used in Government contract work ,Academia and Europe.
- Both are
 - IEEE standards
 - Supported by ASIC(Application-specific integrated circuit) & FPGA synthesis tools

Advantages of HDLs

- Descriptions are portable & independent of technology
 - Allows for easy modification and reuse of previous designs
- Efficient utilization
 - Simply resynthesize
 - New implementation is faster (Design is the same)
 - Decreases design cycle time
- Automatic synthesis of HDL into a working implementation
 - Bypasses some steps such as manual minimization techniques
- Testing
 - Behavioral description can be quickly & easily synthesized prior to implementation
 - Very advantageous early in design process
 - Provides for early evaluation of alternative structures

HDL Use in Design Tools & the Design Process

- Design Entry
- Design Verification
- Test Generation
- Fault Analysis & Simulation
- Timing Analysis & Verification
- Synthesis
- Automatic Schematic Generation
 - Improves efficiency of design flow by eliminating translations of design description as we move through design process

Digital system Abstractions*

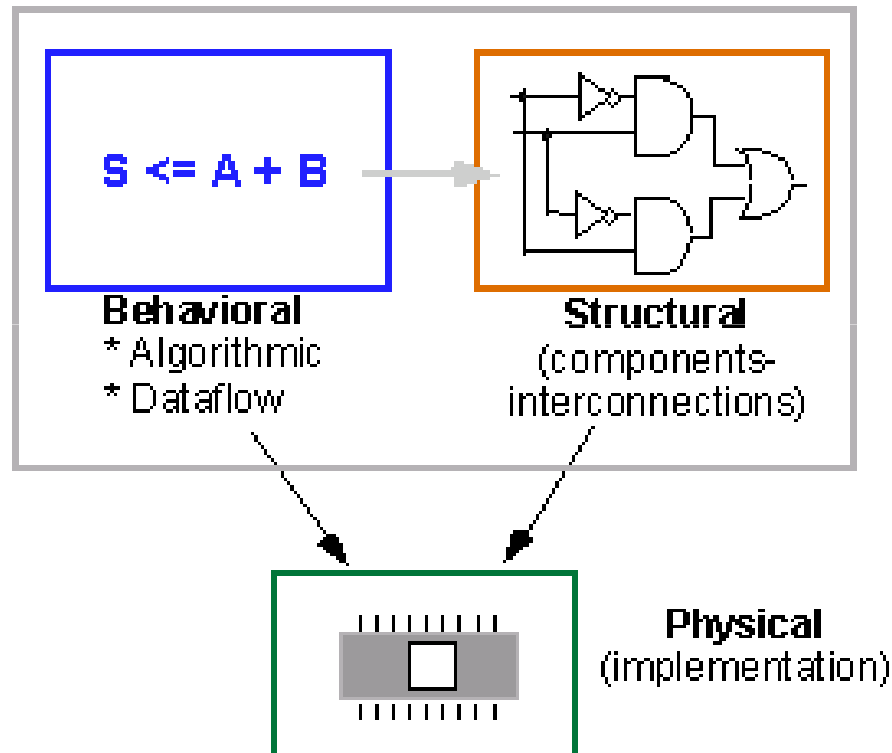


Figure 1: Levels of abstraction: Behavioral, Structural and Physical

Behavioral Modeling

- Abstract description of how the circuit works
- Does not include any indication of structure (implementation) details
- Useful early in design process
 - Allows designer to get a sense of circuit's characteristics before embarking on design process.
 - After functionality is well defined, structural design may follow

- Procedural Models

- Synthesis Tools

- Take a behavioral specification & generate the implementation

Structural Modeling

- System is described as a set of modules consisting of:
 - Interface
 - Description
- Modules interconnected to create system

Structural vs. Behavioral

- Behavioral
 - Functional
 - No implementation details

Structural Modeling

- System is described as a set of modules consisting of:
 - Interface:
 - Declares nets & registers which comprise the two fundamental data types in Verilog
 - Nets
 - » **Wire, wired-AND, wired-OR, trireg**
 - » **Used to connect structures (eg. - gates)**
 - Description

- **Basic Module**
 - Basic Module Format


```
module name;
```

```
    Interface
```

```
    Description
```

```
endmodule
```

- **The Full Adder**

 

Basic Module

```
module fulladder();
```

```
    wire w1, w2, w3, w4, s, cout;
```

```
    reg a, b, c;
```

```
    xor
```

```
        g1(w1, a, b),
```

```
        g2(s, w1, c);
```

```
    and
```

```
        g3(w2, c, b),
```


```
        g4(w3, c, a),
```

```
        g5(w4, a, b);
```

```
    or
```

```
        g6(cout, w2, w3, w4);
```

```
endmodule
```

 

- **Comments**

- Comments are preceded by //


- **Creating Ports**

- Port names are known only inside the module


- Declarations

- Input
 - Output
 - Bidirectional

- **Full Adder Module**

 

 
```
module fulladder(a,b,c,s,cout);  
  input a,b,c;  
  output s,cout;  
  xor #1  
    g1(w1, a, b),  
    g2(s, w1, c);  
  and #1  
    g3(w2, c, b),  
    g4(w3, c, a),  
    g5(w4, a, b);  
  or #1  
    g6(cout, w2, w3, w4);  
endmodule
```



- **Instantiation**

 - Modules can be instantiated to complete a design
- 4-bit Ripple Carry Adder




Vectors

- Scalar
 - A single bit net or reg
- Vector
 - A multiple bit net or reg
- Advantage
 - Vectors make for a more natural way of scaling up a design
- Example
 - Consider the 4-bit adder
- Using scalars:
 - $A_3 A_2 A_1 A_0 + B_3 B_2 B_1 B_0 + C_{in} = C_{out} S_3 S_2 S_1 S_0$
- Using vectors:
 - $A + B + C_{in} = C_{out}, S$
 - $A[3:0] + B[3:0] + C_{in} = C_{out}, S[3:0]$

```

module fulladder(a,b,c,s,cout);
input a,b,c;
output s,cout;
xor #1
    g1(w1, a, b),
    g2(s, w1, c);
and #1
    g3(w2, c, b),
    g4(w3, c, a),
    g5(w4, a, b);
or #1
    g6(cout, w2, w3, w4);
endmodule

```

 

```

module fourBitAdder(x,y,s,cout,cin);
input [3:0] x,y;
output [3:0] s;
input cin;
output cout;
wire c[3:0];
fulladder f0 (x[0],y[0],cin,s[0],c[0]);
fulladder f1 (x[1],y[1],c[0],s[1],c[1]);
fulladder f2 (x[2],y[2],c[1],s[2],c[2]);
fulladder f3 (x[3],y[3],c[2],s[3],cout);
endmodule

```


References

- Donald E. Thomas and Philip R. Moorby, *The Verilog Hardware Description Language*, Kluwer Academic Publishers, 1998
- Samir Palnitkar, *Verilog HDL A Guide to Digital Design and Synthesis*, Prentice Hall, Inc., 4th Edition, 1996
- David R. Smith and Paul D. Franzon, *Verilog Styles of Digital Systems*, Prentice Hall, Inc., 2000
- Michael D. Ciletti, *Advanced Digital Design with the Verilog HDL*, Pearson Education, Inc. (Prentice Hall), 2003
- * VHDL Tutorial, Jan Van der Spiegel, University of Pennsylvania, Department of Electrical and Systems Engineering
- Wikipedia